
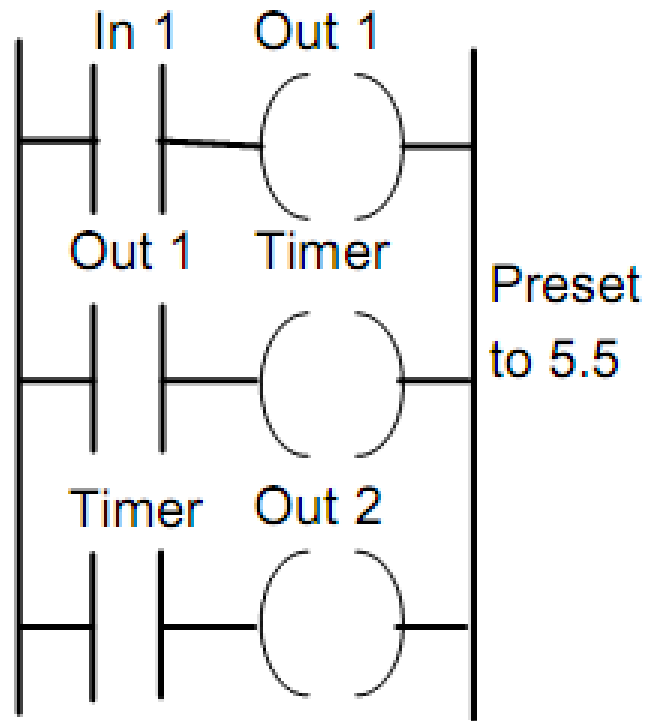


# Timers (cont.)

- Sequencing

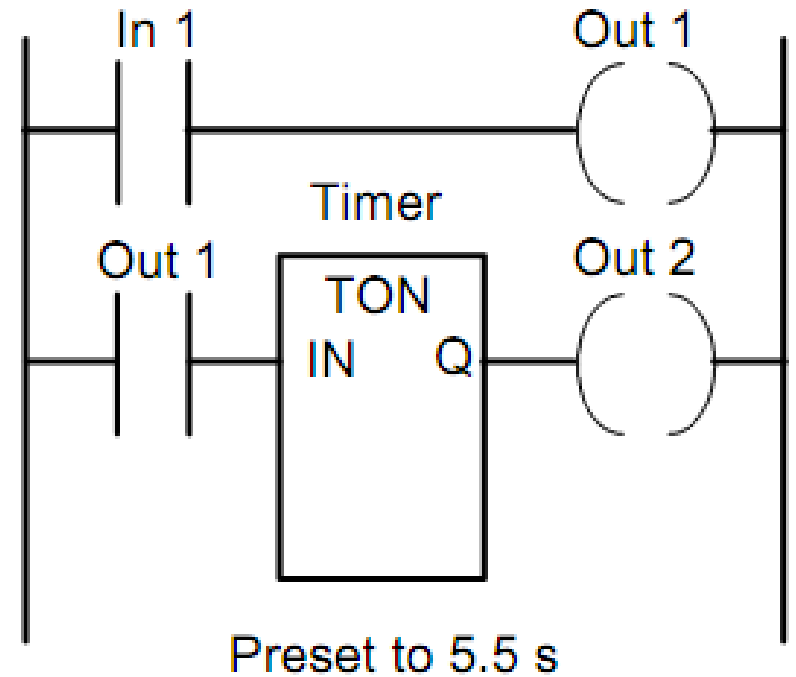



(a)




(b)

# Timers can be start three outputs


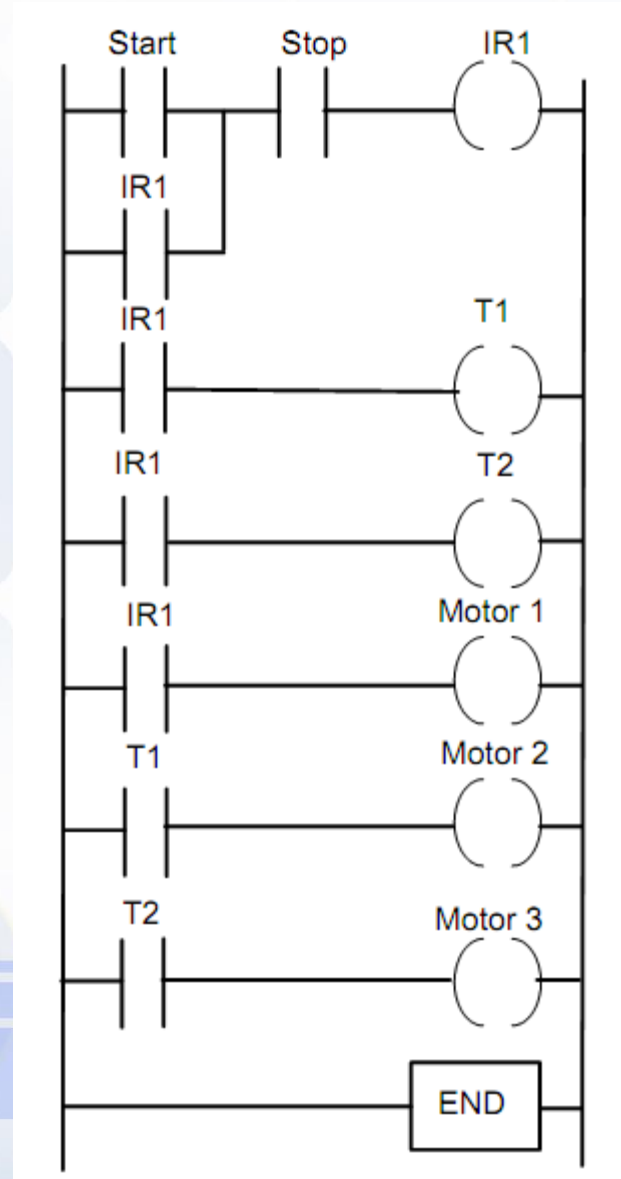


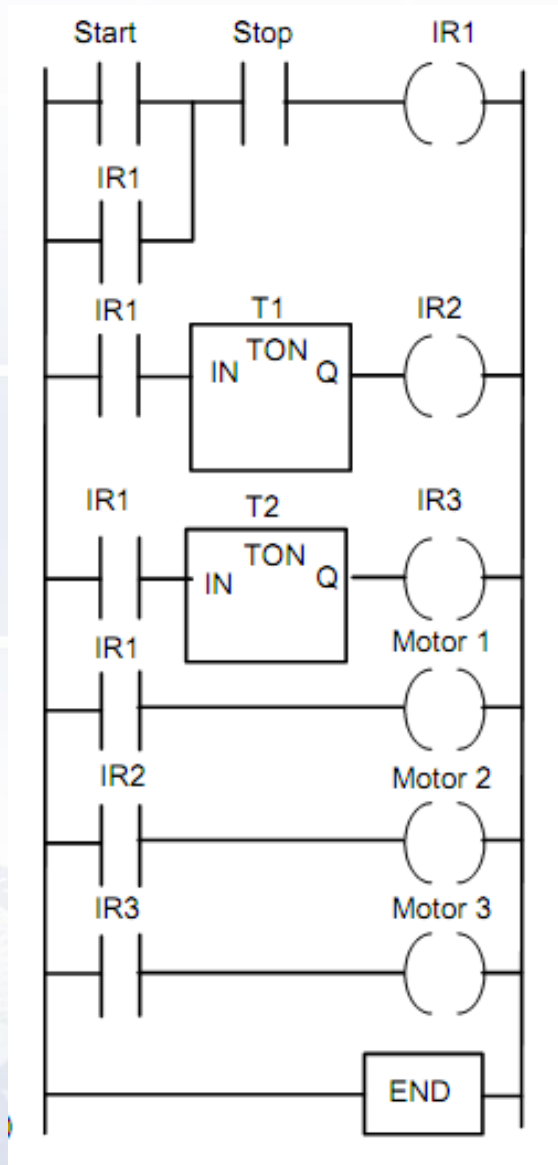

- Cascaded Timers

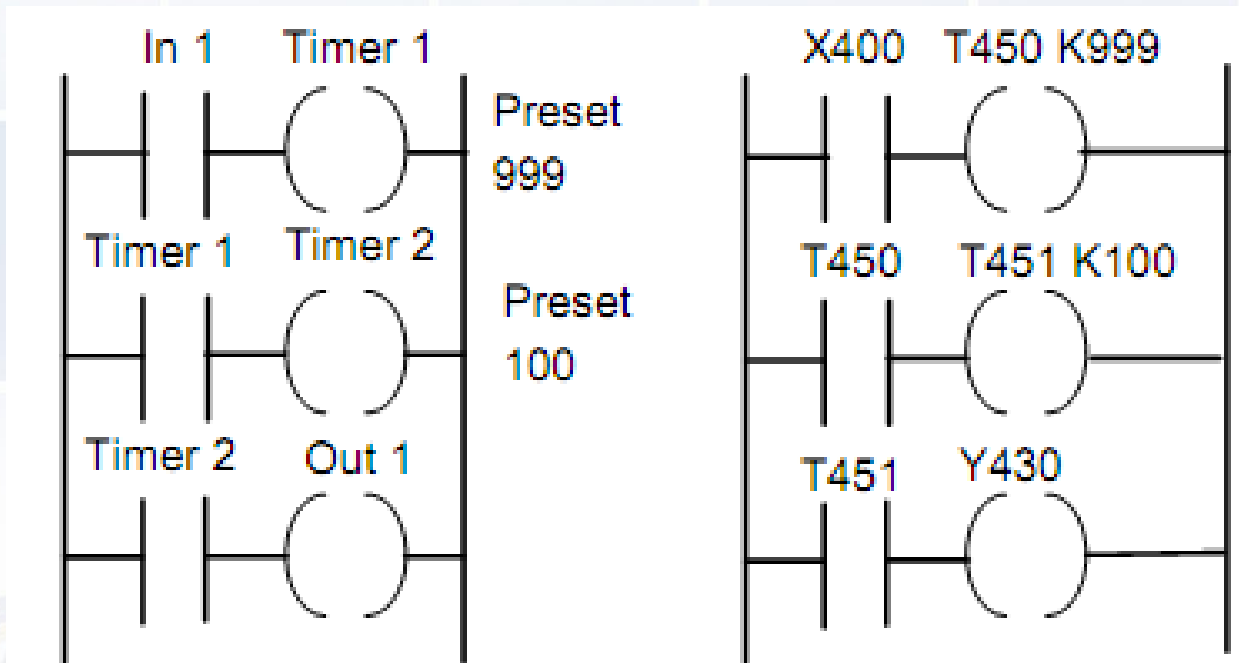


- Off Delay timers

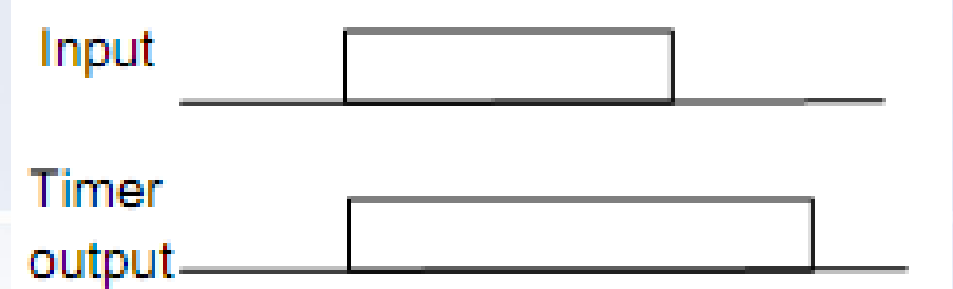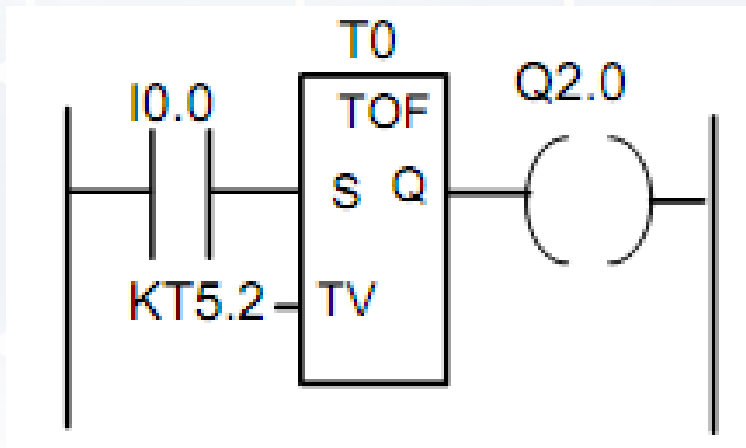

Siemens



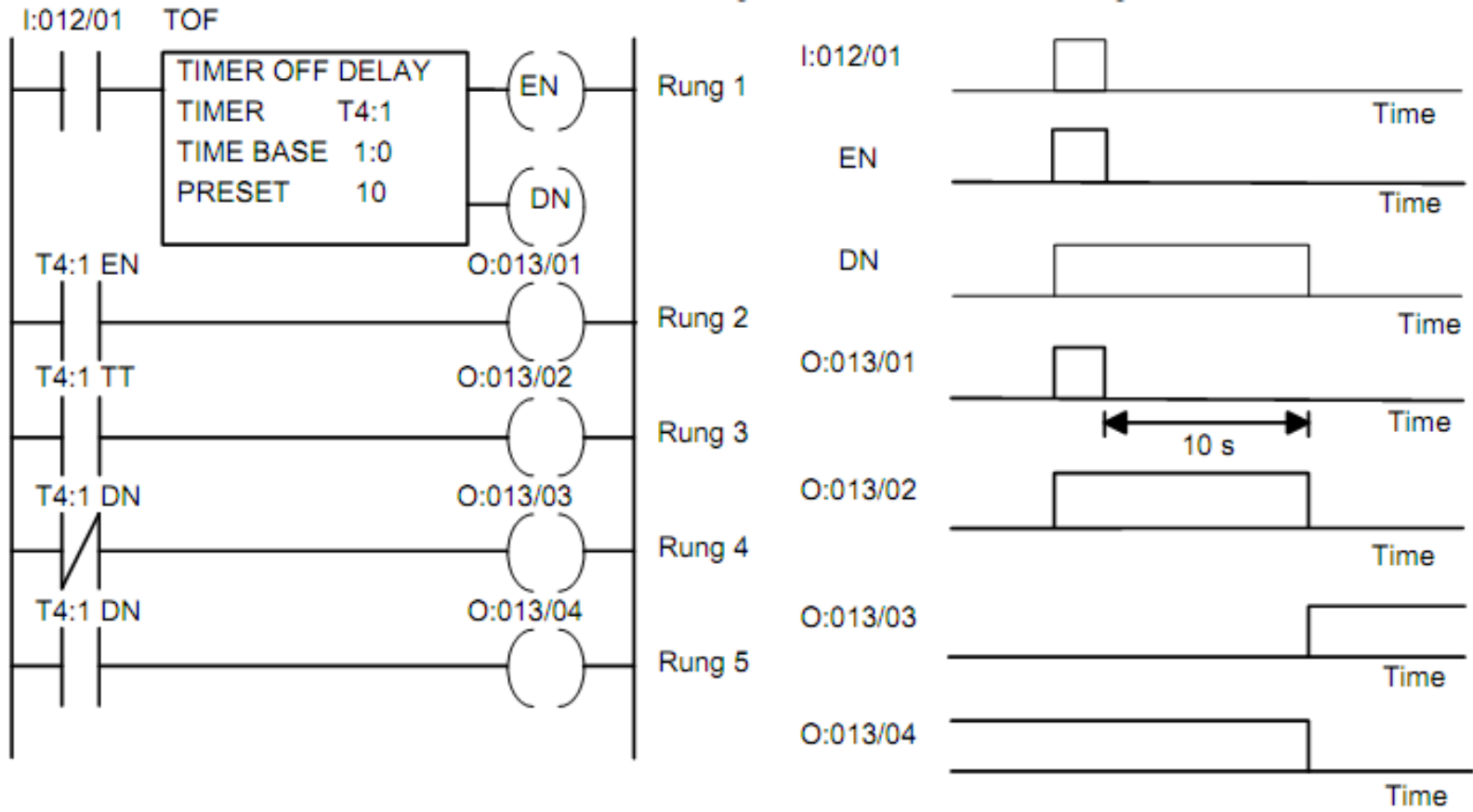

# Allen-Bradley