

Listrik DC


Kirchoff's Laws

Circuit Definitions

- **Node** – any point where 2 or more circuit elements are connected together
 - Wires usually have negligible resistance
 - Each node has one voltage (w.r.t. ground)
- **Branch** – a circuit element between two nodes
- **Loop** – a collection of branches that form a closed path returning to the same node without going through any other nodes or branches twice


Example

- How many nodes, branches & loops?

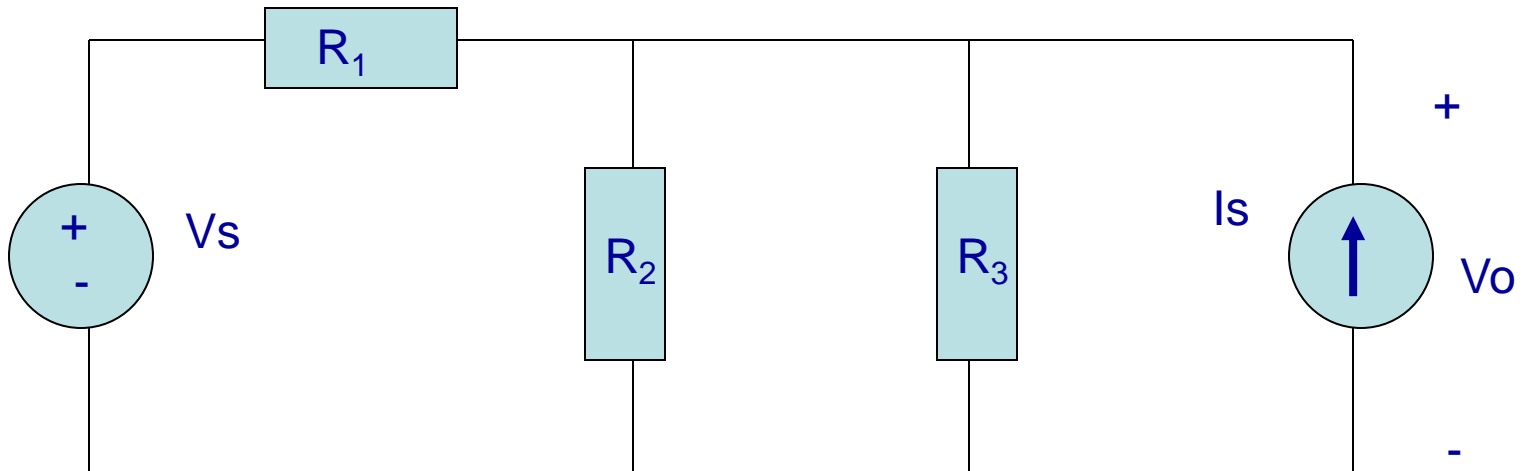


Example

- Three nodes

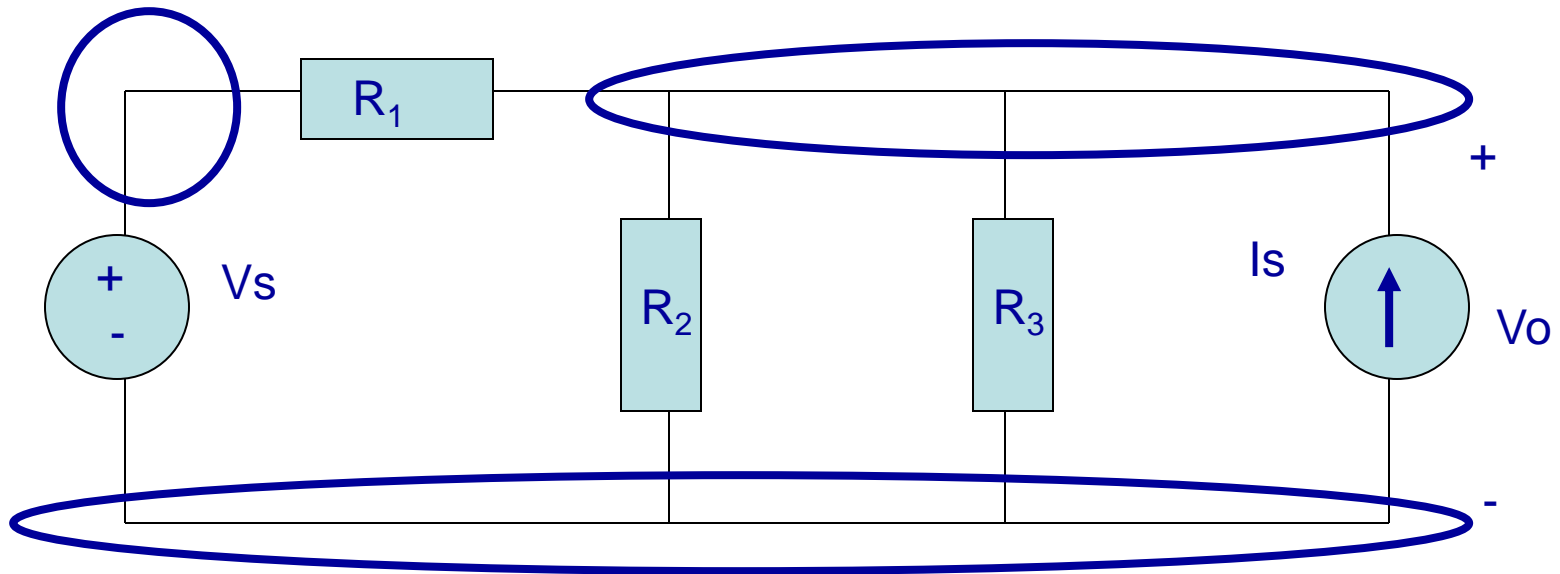


Example

- 5 Branches

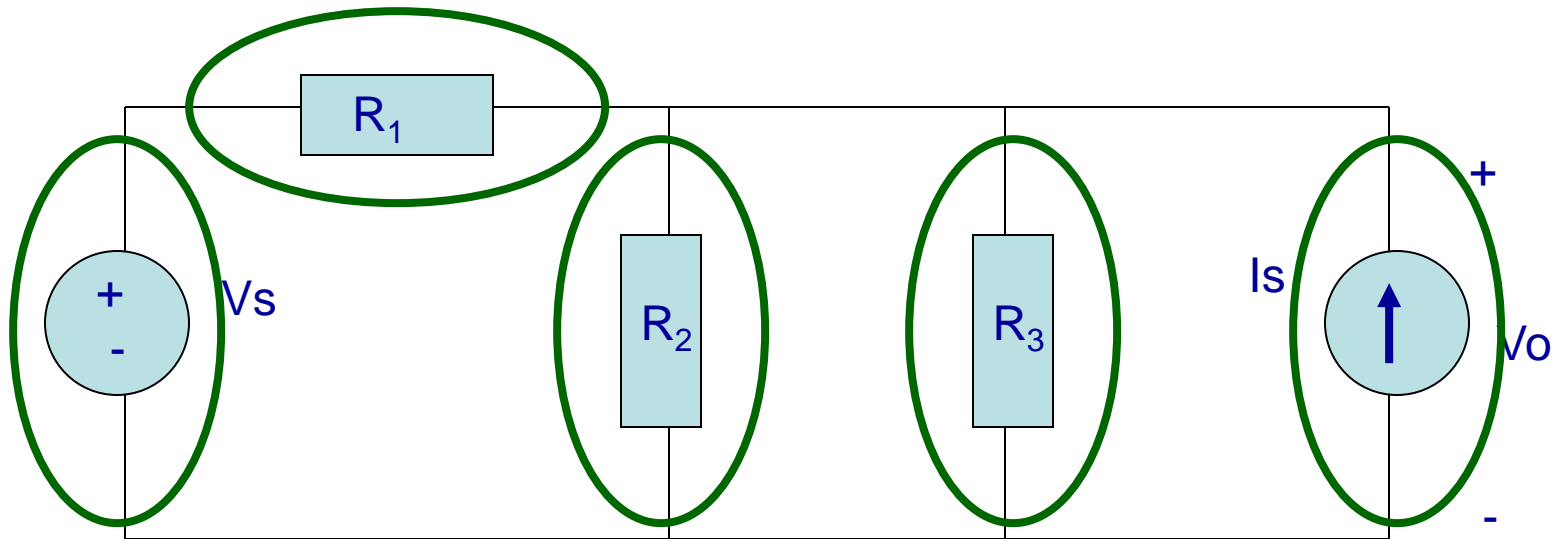

Example

- Three Loops, if starting at node A

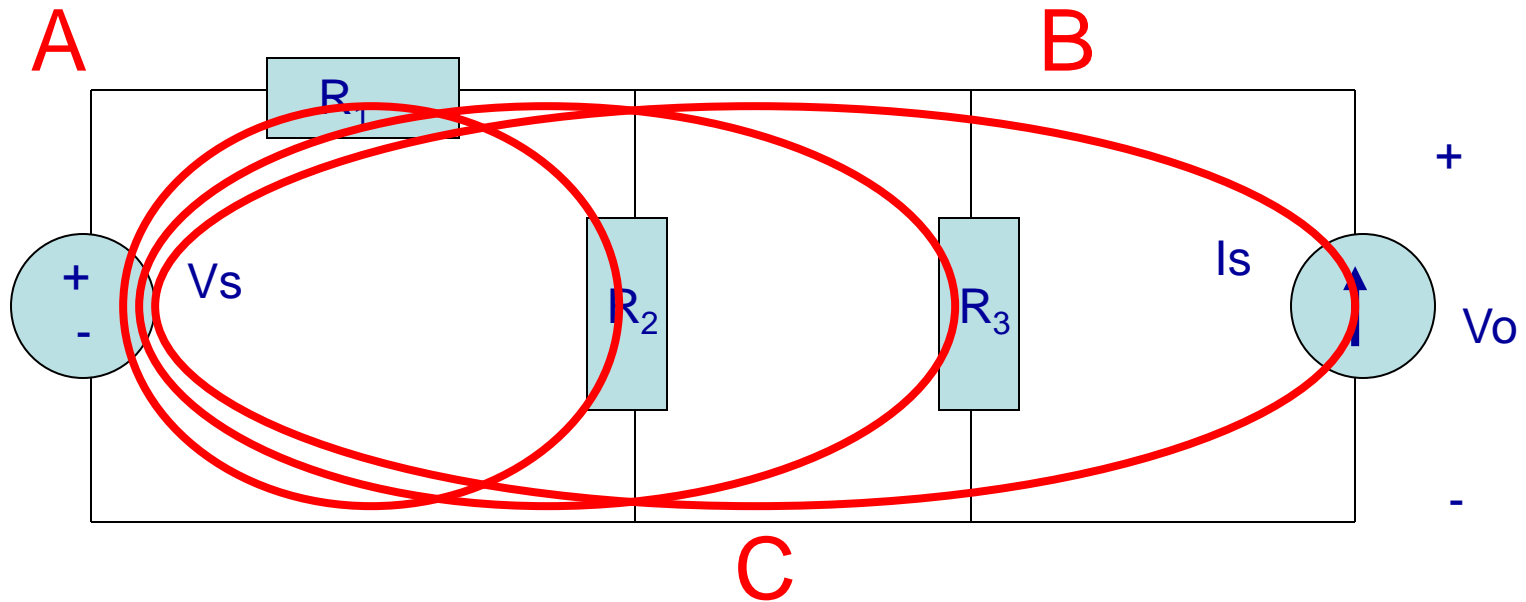


Kirchoff's Voltage Law (KVL)

- The algebraic sum of voltages around each loop is zero
 - Beginning with one node, add voltages across each branch in the loop (if you encounter a + sign first) and subtract voltages (if you encounter a – sign first)
- Σ voltage drops - Σ voltage rises = 0
- Or Σ voltage drops = Σ voltage rises

Example

- Kirchoff's Voltage Law around 1st Loop

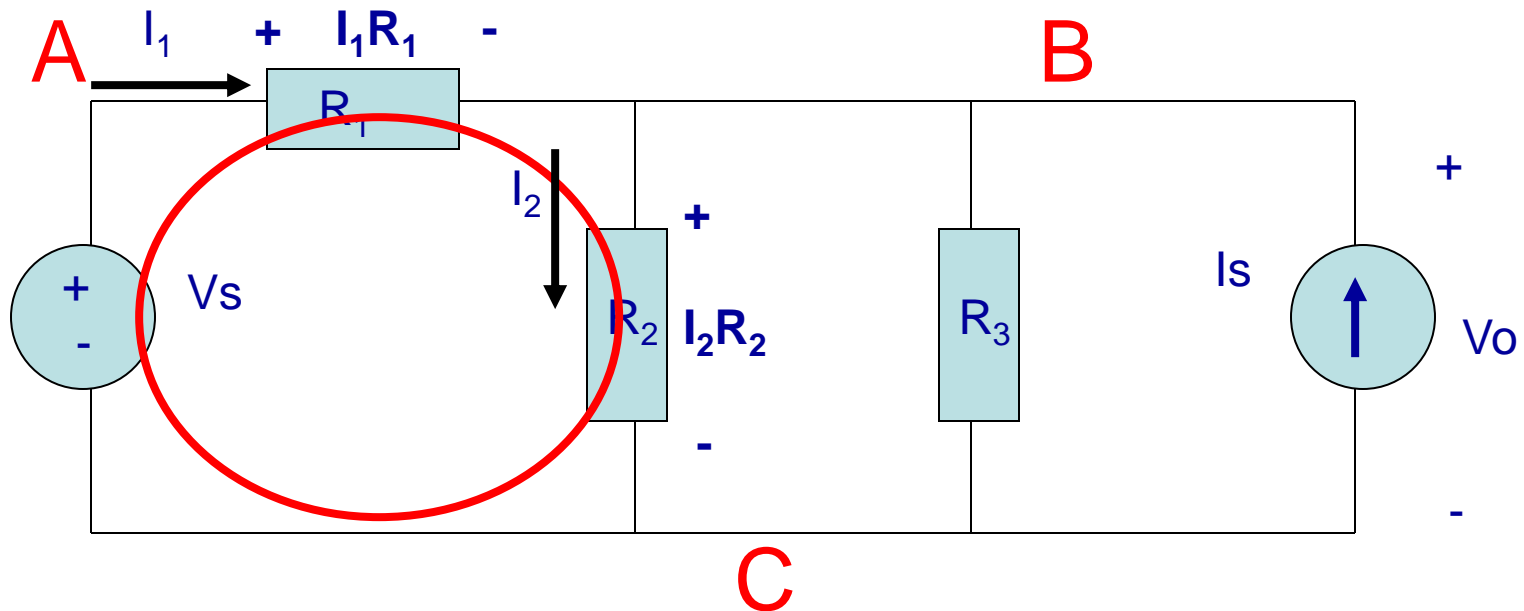


Assign current variables and directions

Use Ohm's law to assign voltages and polarities consistent with passive devices (current enters at the + side)

Example


- Kirchoff's Voltage Law around 1st Loop

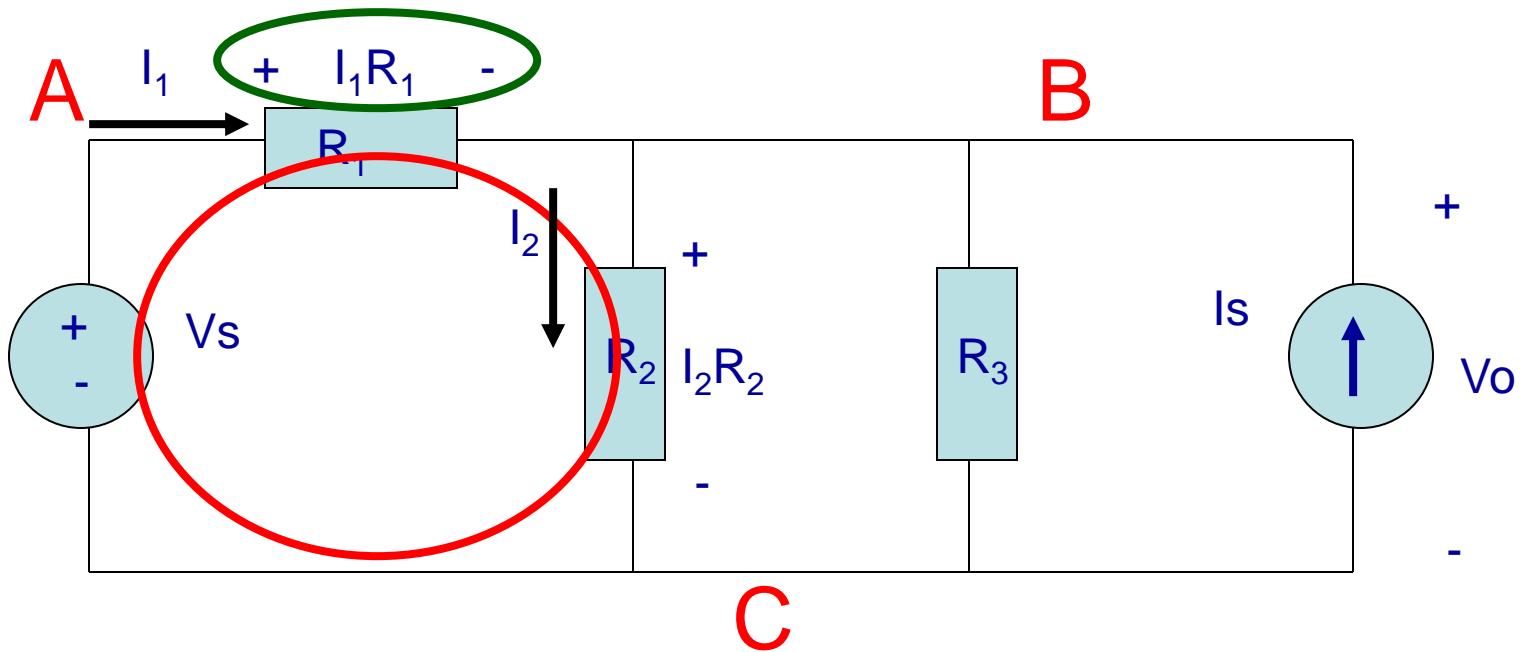

Starting at node A, add the 1st voltage drop: $+ I_1 R_1$

Example


- Kirchoff's Voltage Law around 1st Loop

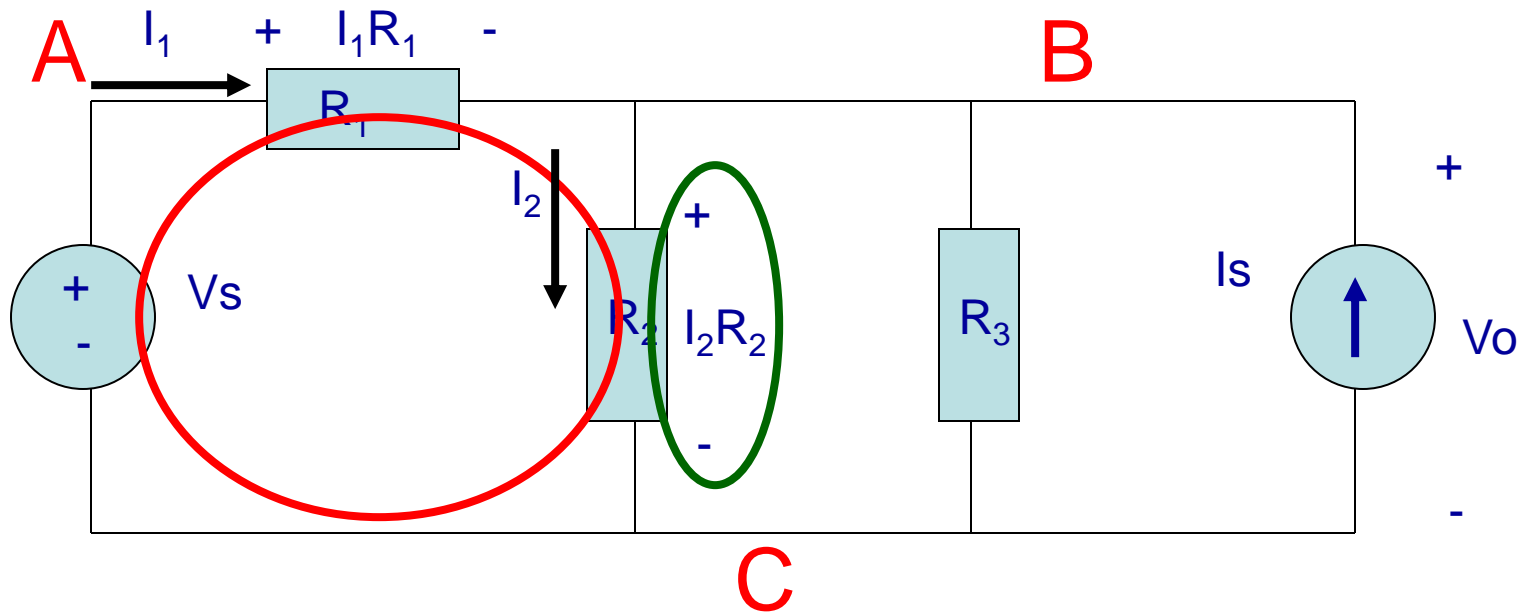

Add the voltage drop from B to C through R_2 : $+ I_1 R_1 + I_2 R_2$

Example


- Kirchoff's Voltage Law around 1st Loop

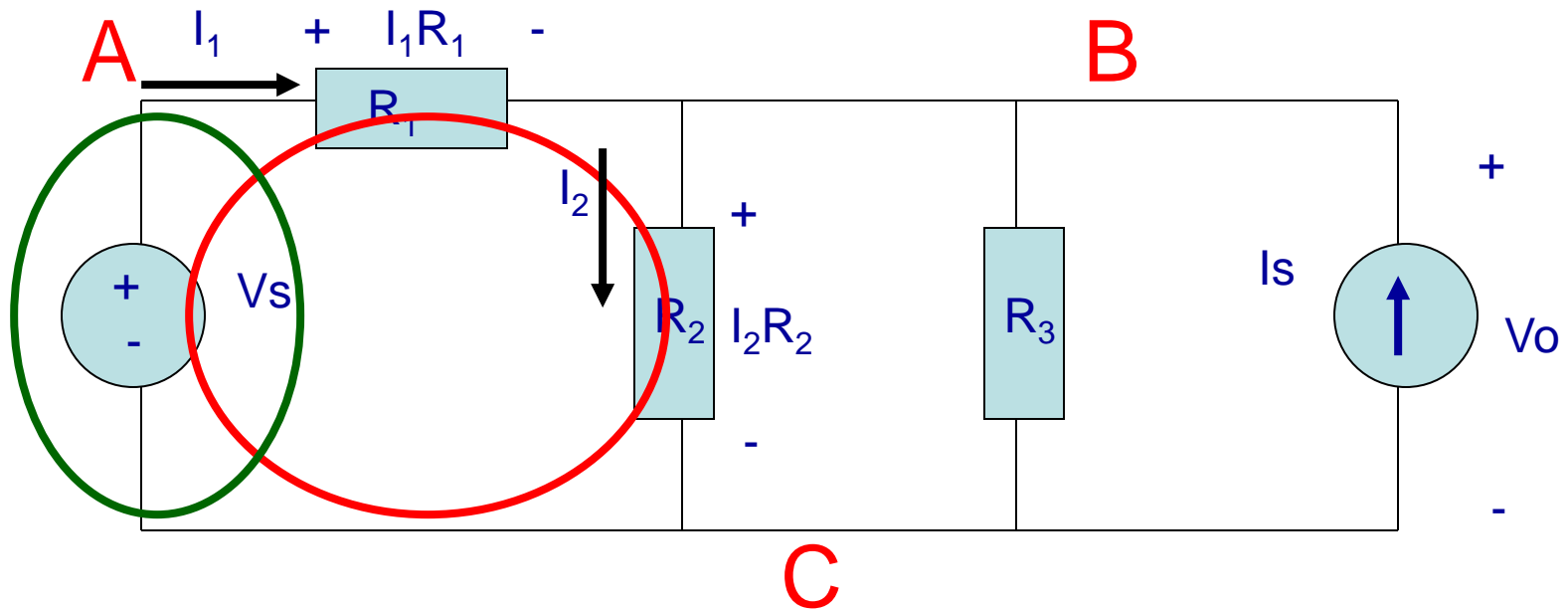

Subtract the voltage rise from C to A through V_s : $+ I_1 R_1 + I_2 R_2 - V_s = 0$
Notice that the sign of each term matches the polarity encountered 1st


Circuit Analysis

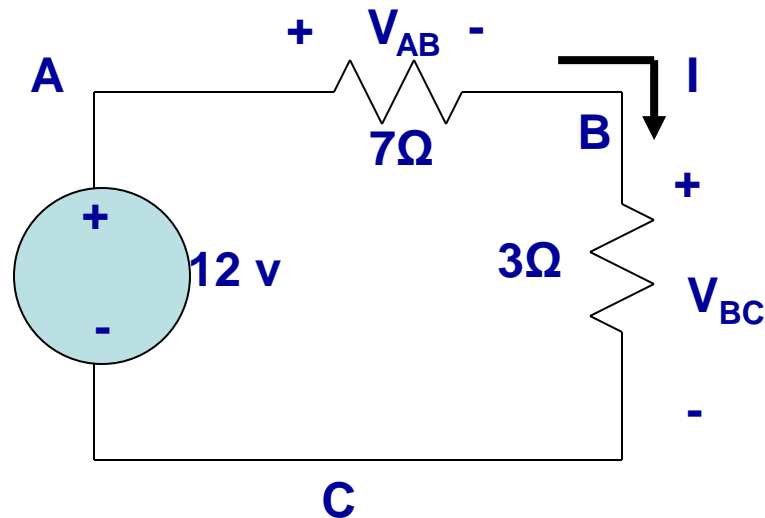- When given a circuit with sources and resistors having fixed values, you can use Kirchoff's two laws and Ohm's law to determine all branch voltages and currents




Circuit Analysis

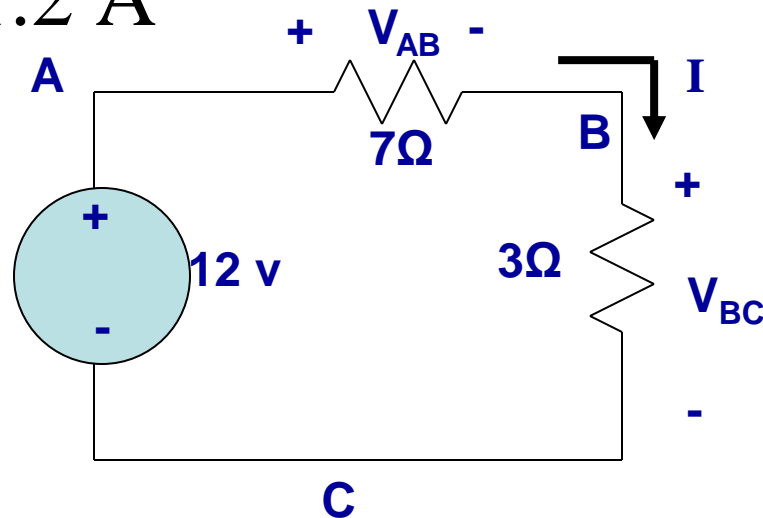- By Ohm's law: $V_{AB} = I \cdot 7\Omega$ and $V_{BC} = I \cdot 3\Omega$
- By KVL: $V_{AB} + V_{BC} - 12\text{ v} = 0$
- Substituting: $I \cdot 7\Omega + I \cdot 3\Omega - 12\text{ v} = 0$
- Solving: $I = 1.2\text{ A}$




Circuit Analysis

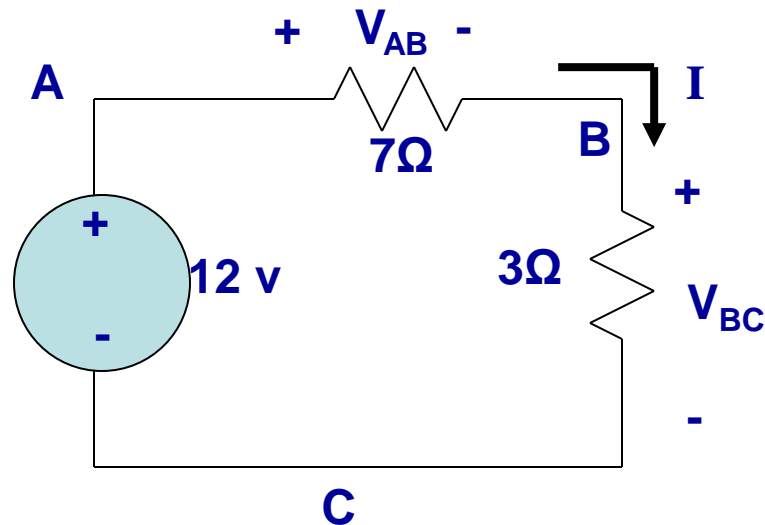- Since $V_{AB} = I \cdot 7\Omega$ and $V_{BC} = I \cdot 3\Omega$
- And $I = 1.2 \text{ A}$
- So $V_{AB} = 8.4 \text{ v}$ and $V_{BC} = 3.6 \text{ v}$




Series Resistors

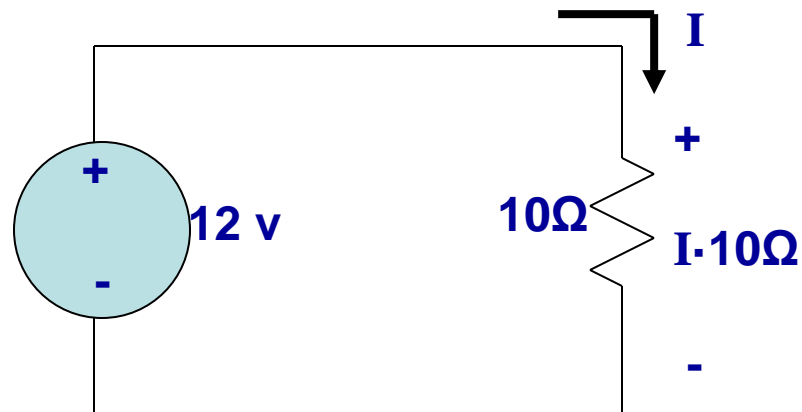- KVL: $+I \cdot 10\Omega - 12\text{ v} = 0$, So $I = 1.2\text{ A}$
- From the viewpoint of the source, the 7 and 3 ohm resistors in series are equivalent to the 10 ohms



Series Resistors

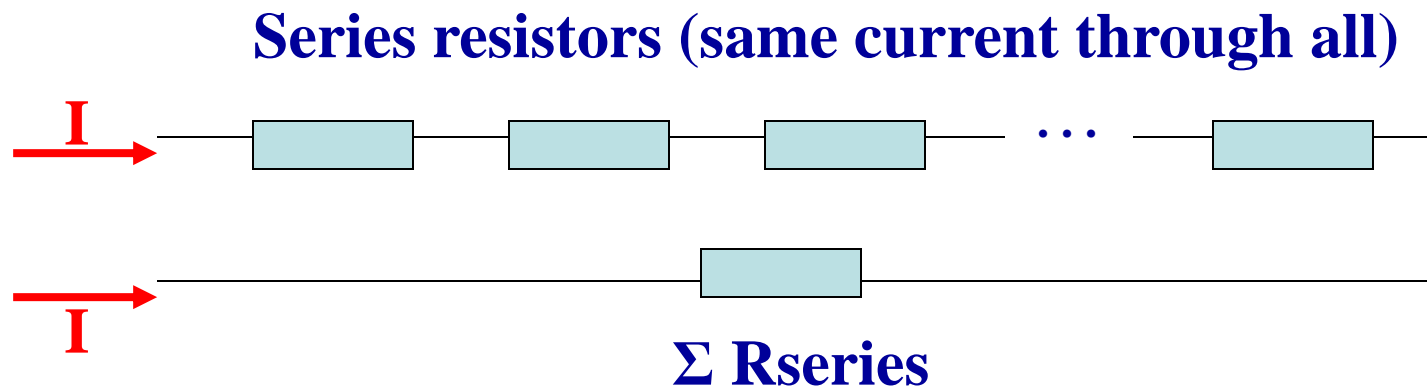- To the rest of the circuit, series resistors can be replaced by an equivalent resistance equal to the sum of all resistors




Kirchoff's Current Law (KCL)

- The algebraic sum of currents entering a node is zero
 - Add each branch current entering the node and subtract each branch current leaving the node
- $\sum \text{currents in} - \sum \text{currents out} = 0$
- Or $\sum \text{currents in} = \sum \text{currents out}$

Example


- Kirchoff's Current Law at B

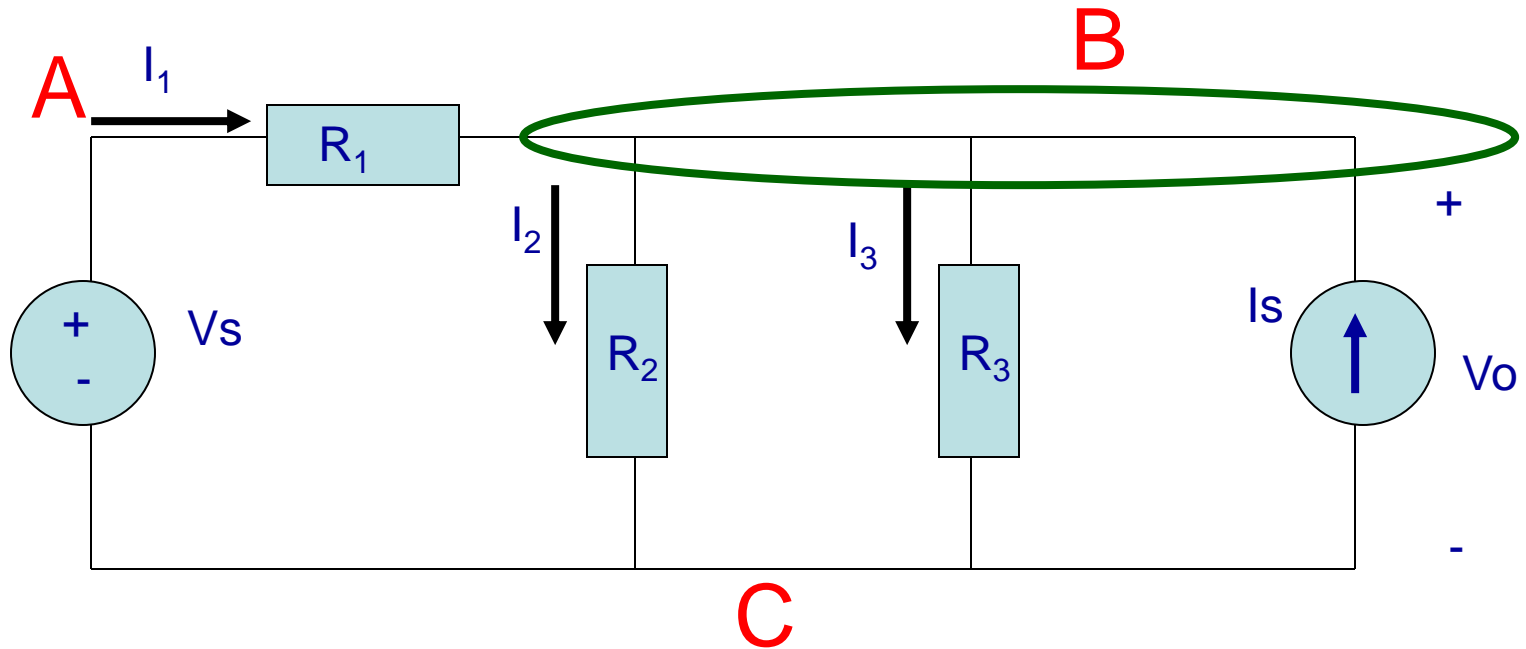

Assign current variables and directions

Add currents in, subtract currents out: $I_1 - I_2 - I_3 + I_s = 0$

Circuit Analysis

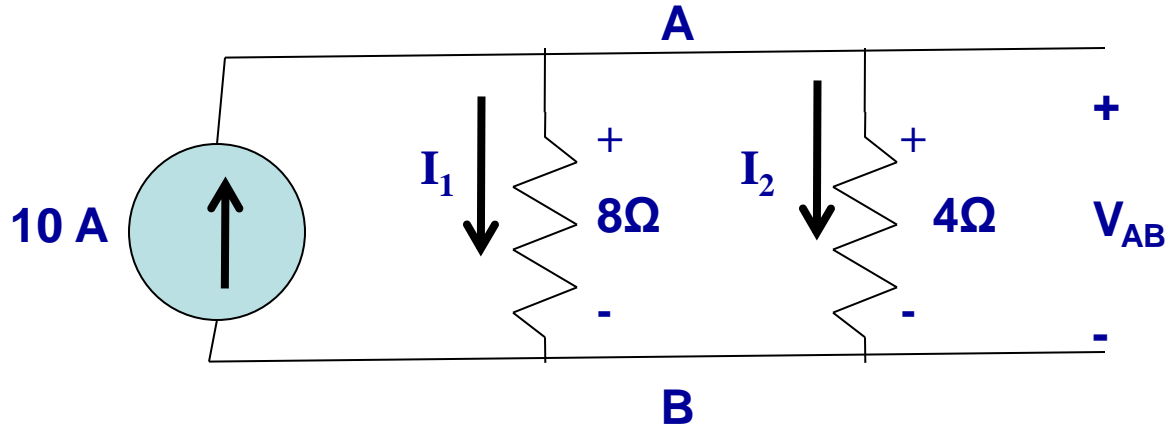

By KVL: $-I_1 \cdot 8\Omega + I_2 \cdot 4\Omega = 0$

Solving: $I_2 = 2 \cdot I_1$


By KCL: $10A = I_1 + I_2$

Substituting: $10A = I_1 + 2 \cdot I_1 = 3 \cdot I_1$

So $I_1 = 3.33 A$ and $I_2 = 6.67 A$

And $V_{AB} = 26.33$ volts

Circuit Analysis

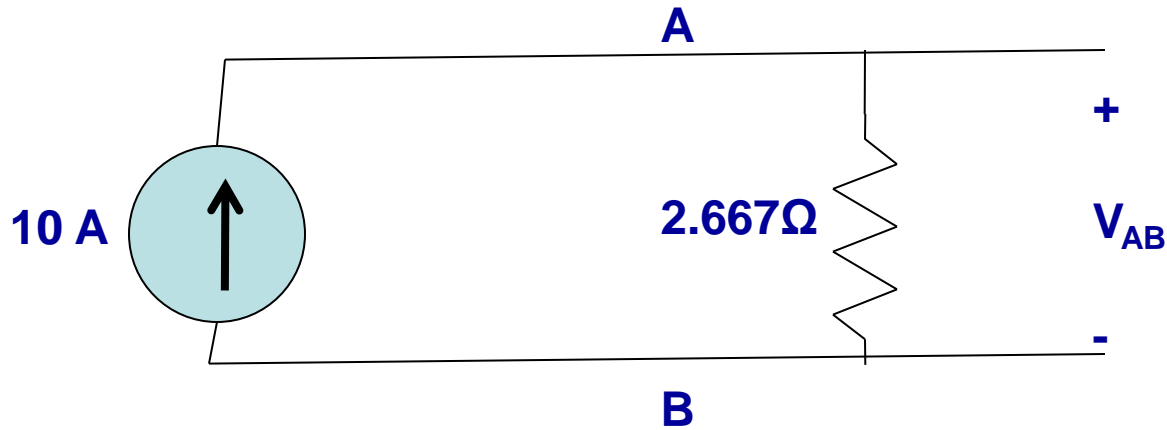

By Ohm's Law: $V_{AB} = 10 \text{ A} \cdot 2.667 \text{ } \Omega$

So $V_{AB} = 26.67 \text{ volts}$

Replacing two parallel resistors (8 and 4 Ω) by one equivalent one produces the same result from the viewpoint of the rest of the circuit.

Parallel Resistors


- The equivalent resistance for any number of resistors in parallel (i.e. they have the same voltage across each resistor):

$$R_{eq} = \frac{1}{1/R_1 + 1/R_2 + \dots + 1/R_N}$$

- For two parallel resistors:


$$R_{eq} = R_1 \cdot R_2 / (R_1 + R_2)$$

Example Circuit

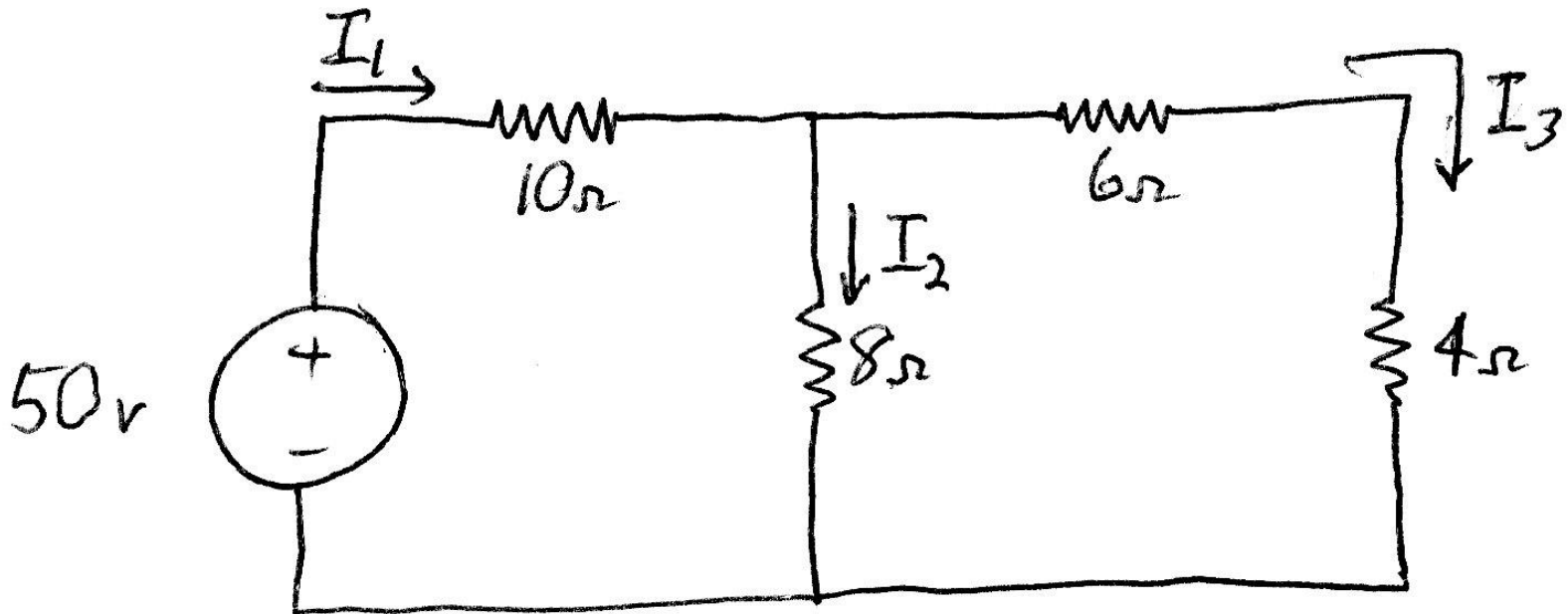


**Solve for the currents through each resistor
And the voltages across each resistor**

Example Circuit

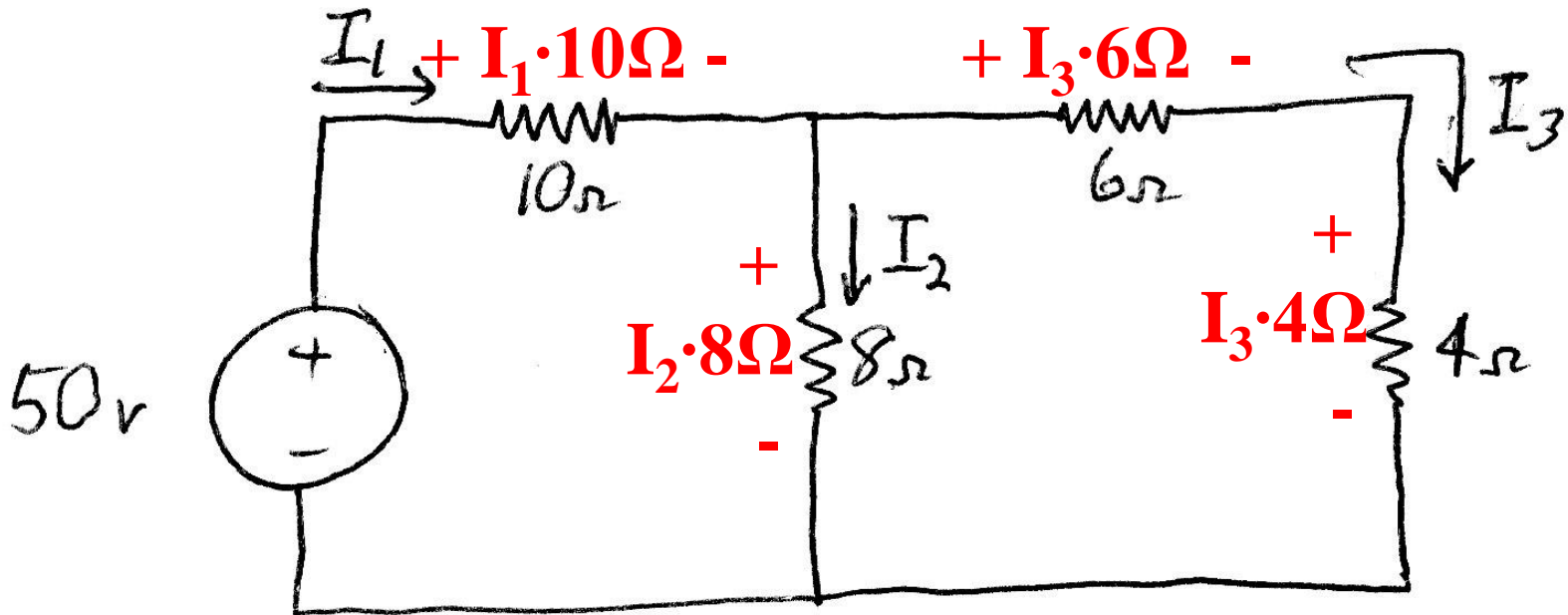


Using Ohm's law, add polarities and expressions for each resistor voltage

Example Circuit

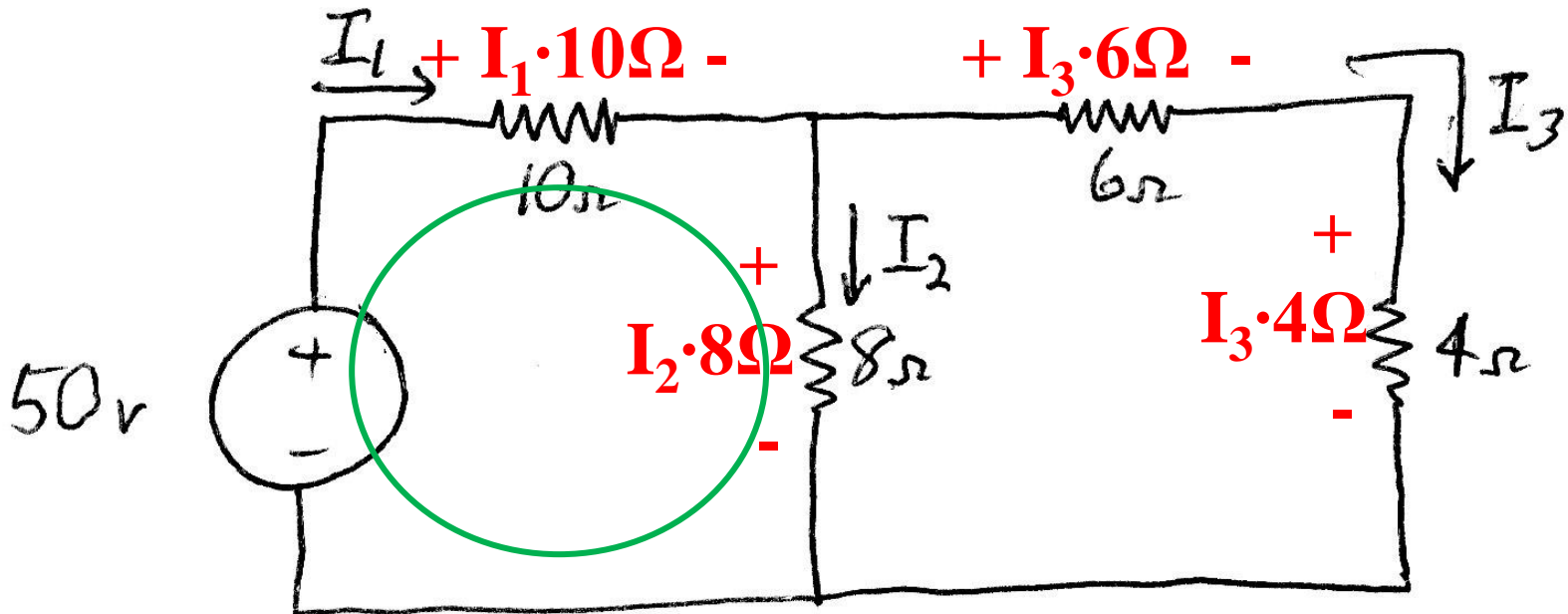

Write 1st Kirchoff's voltage law equation
 $-50 \text{ v} + I_1 \cdot 10\Omega + I_2 \cdot 8\Omega = 0$

Example Circuit

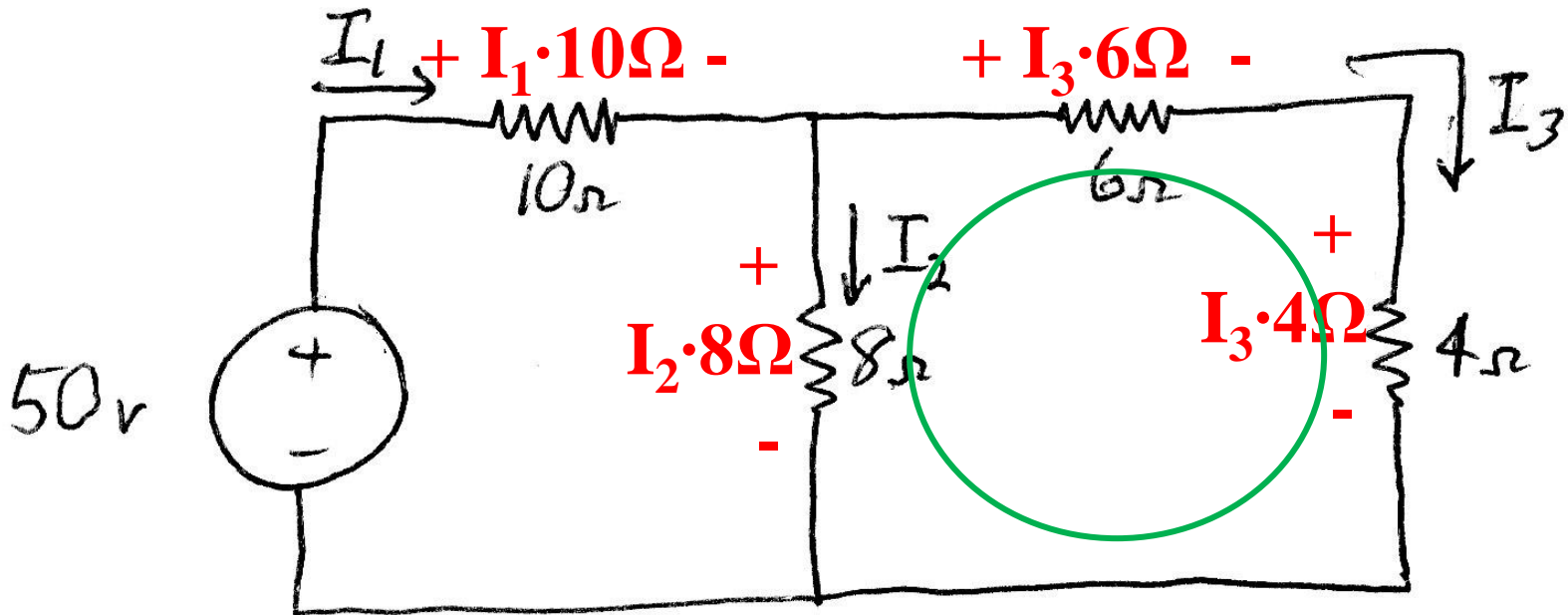


Write 2nd Kirchoff's voltage law equation

$$-I_2 \cdot 8\Omega + I_3 \cdot 6\Omega + I_3 \cdot 4\Omega = 0$$

$$\text{or } I_2 = I_3 \cdot (6+4)/8 = 1.25 \cdot I_3$$

Example Circuit

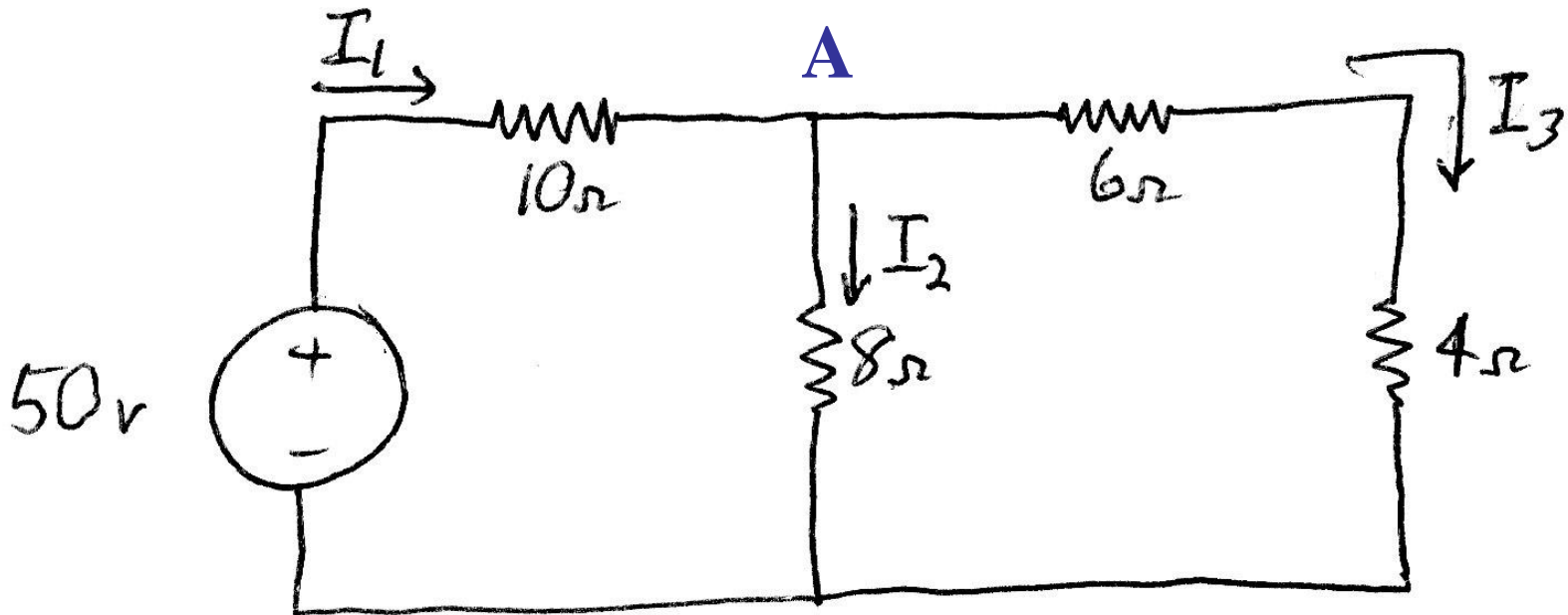

Write Kirchoff's current law equation at A
 $+I_1 - I_2 - I_3 = 0$

Example Circuit

- We now have 3 equations in 3 unknowns, so we can solve for the currents through each resistor, that are used to find the voltage across each resistor
- Since $I_1 - I_2 - I_3 = 0$, $I_1 = I_2 + I_3$
- Substituting into the 1st KVL equation
$$-50 \text{ v} + (I_2 + I_3) \cdot 10\Omega + I_2 \cdot 8\Omega = 0$$
or $I_2 \cdot 18 \Omega + I_3 \cdot 10 \Omega = 50 \text{ volts}$


Example Circuit

- But from the 2nd KVL equation, $I_2 = 1.25 \cdot I_3$
- Substituting into 1st KVL equation:
 $(1.25 \cdot I_3) \cdot 18 \Omega + I_3 \cdot 10 \Omega = 50 \text{ volts}$
Or: $I_3 \cdot 22.5 \Omega + I_3 \cdot 10 \Omega = 50 \text{ volts}$
Or: $I_3 \cdot 32.5 \Omega = 50 \text{ volts}$
Or: $I_3 = 50 \text{ volts} / 32.5 \Omega$
Or: $I_3 = 1.538 \text{ amps}$

Example Circuit


- Since $I_3 = 1.538$ amps
 $I_2 = 1.25 \cdot I_3 = 1.923$ amps
- Since $I_1 = I_2 + I_3$, $I_1 = 3.461$ amps
- The voltages across the resistors:
 $I_1 \cdot 10\Omega = 34.61$ volts
 $I_2 \cdot 8\Omega = 15.38$ volts
 $I_3 \cdot 6\Omega = 9.23$ volts
 $I_3 \cdot 4\Omega = 6.15$ volts

Example Circuit

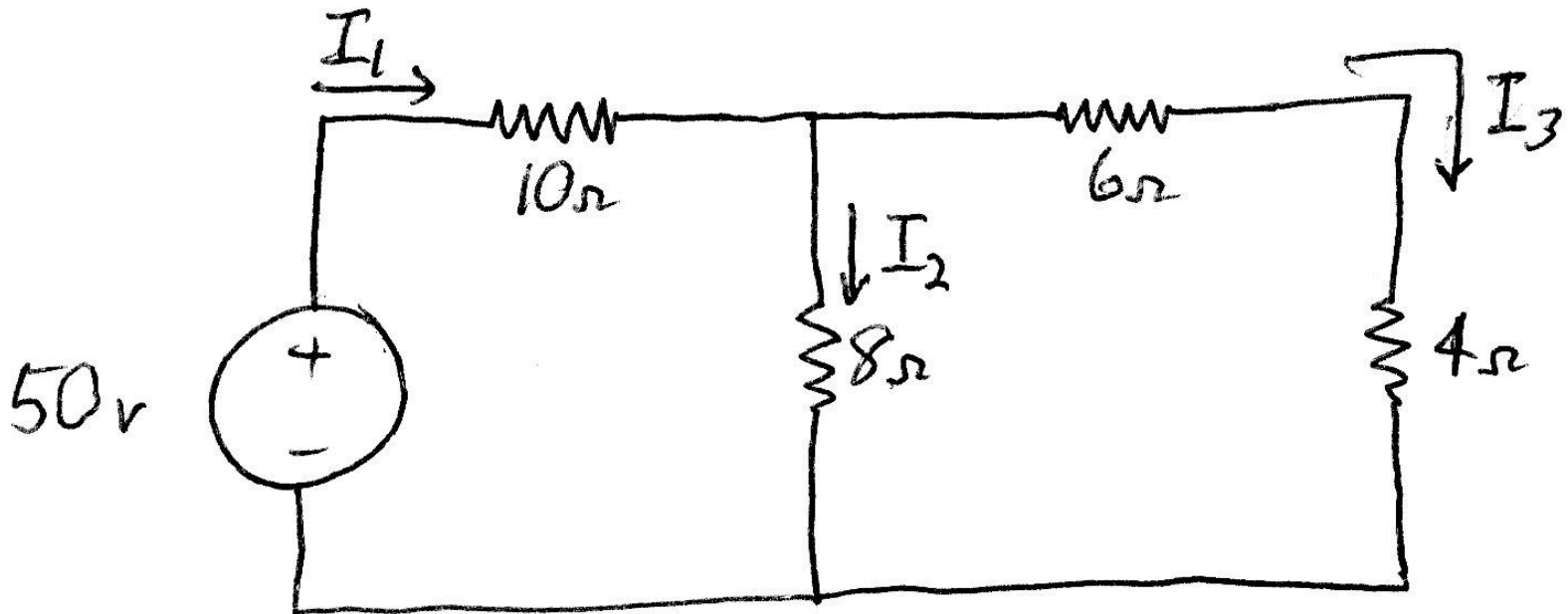


**Solve for the currents through each resistor
And the voltages across each resistor using
Series and parallel simplification.**

Example Circuit

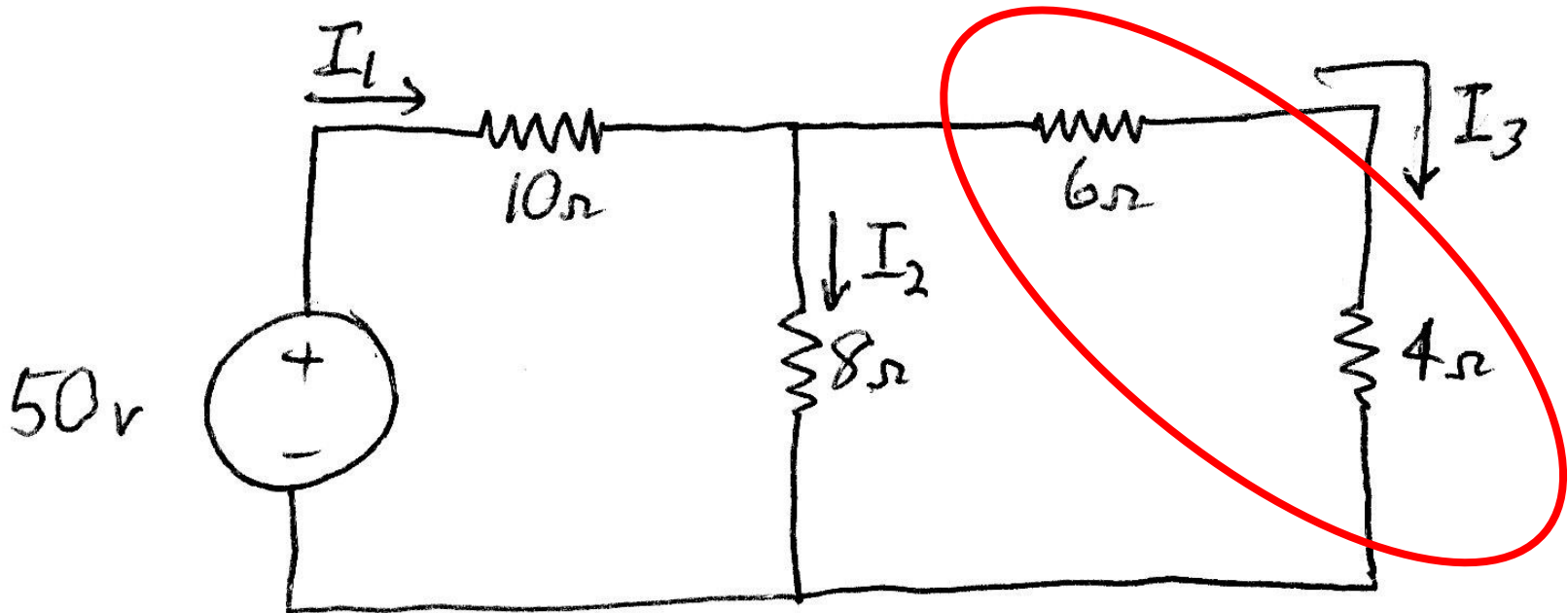


The 6 and 4 ohm resistors are in series, so are combined into $6+4 = 10\Omega$

Example Circuit

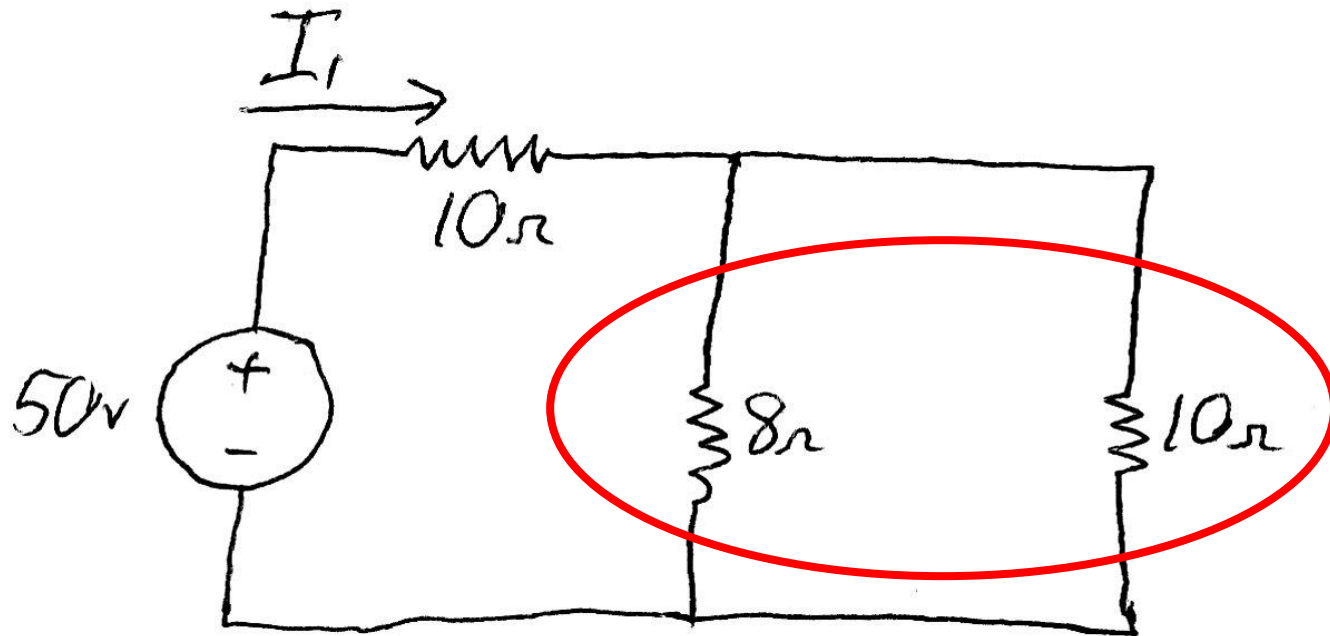


The 8 and 10 ohm resistors are in parallel, so are combined into $8 \cdot 10 / (8 + 10) = 14.4 \Omega$

Example Circuit

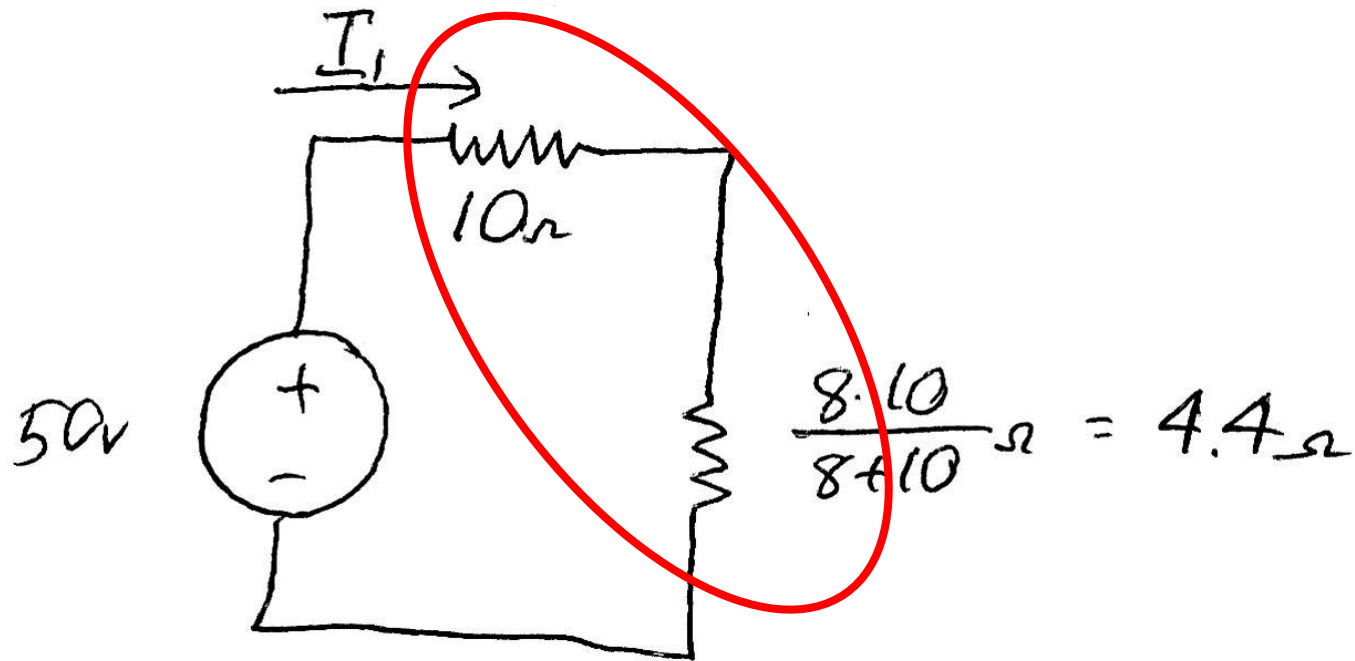

The 10 and 4.4 ohm resistors are in series, so are combined into $10+4 = 14.4\Omega$


Example Circuit

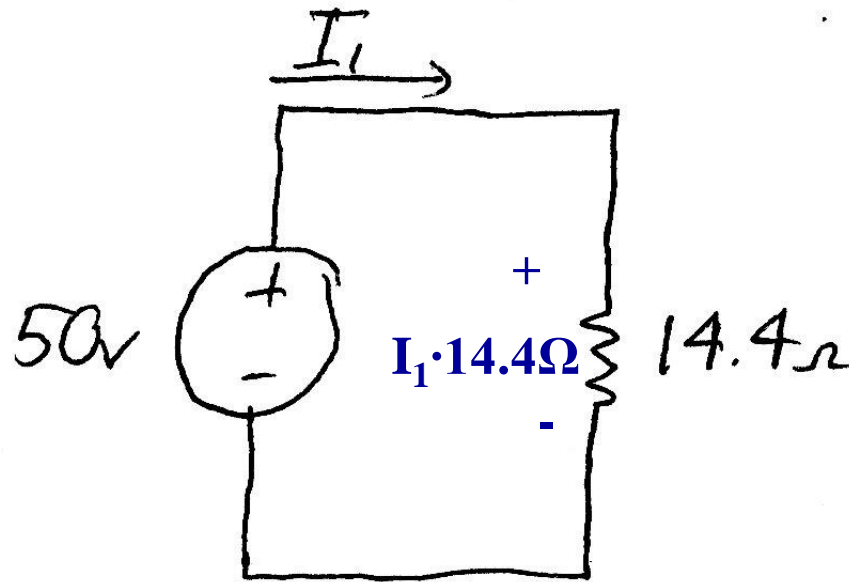

Writing KVL, $I_1 \cdot 14.4\Omega - 50 \text{ v} = 0$

Or $I_1 = 50 \text{ v} / 14.4\Omega = 3.46 \text{ A}$


Example Circuit

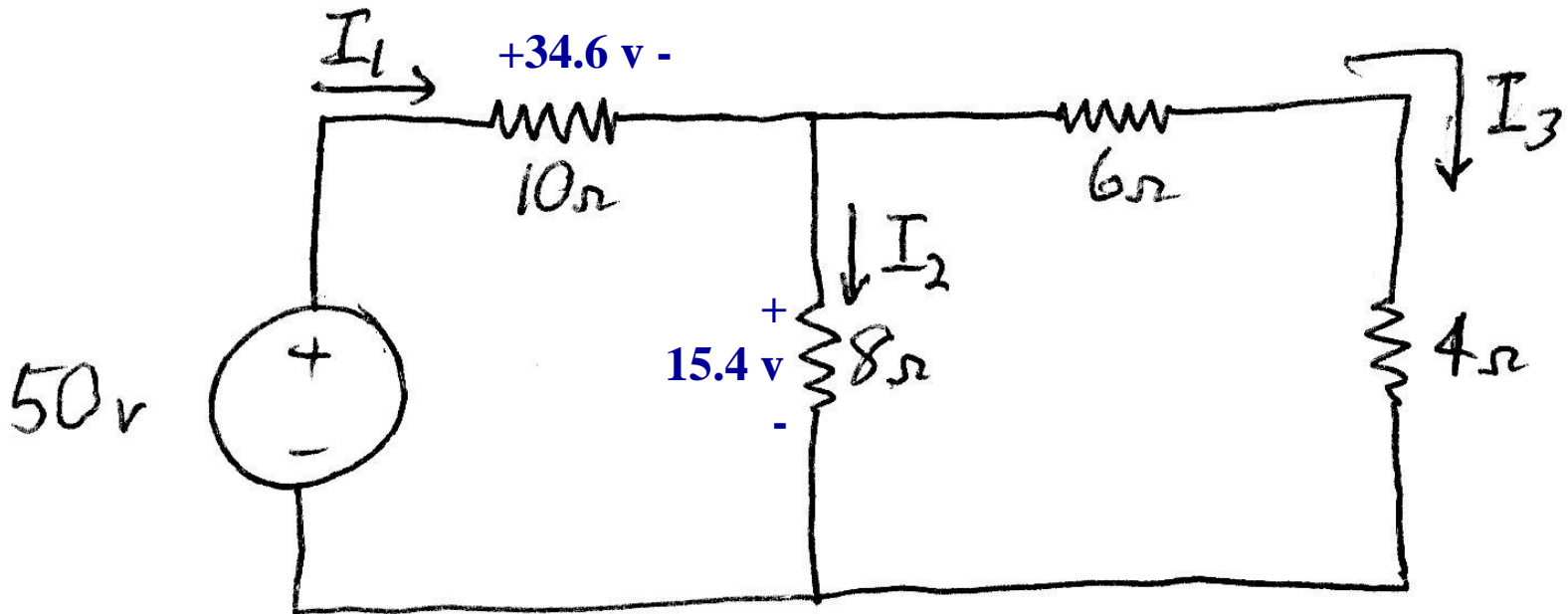

If $I_1 = 3.46$ A, then $I_1 \cdot 10 \Omega = 34.6$ v

So the voltage across the $8 \Omega = 15.4$ v

Example Circuit

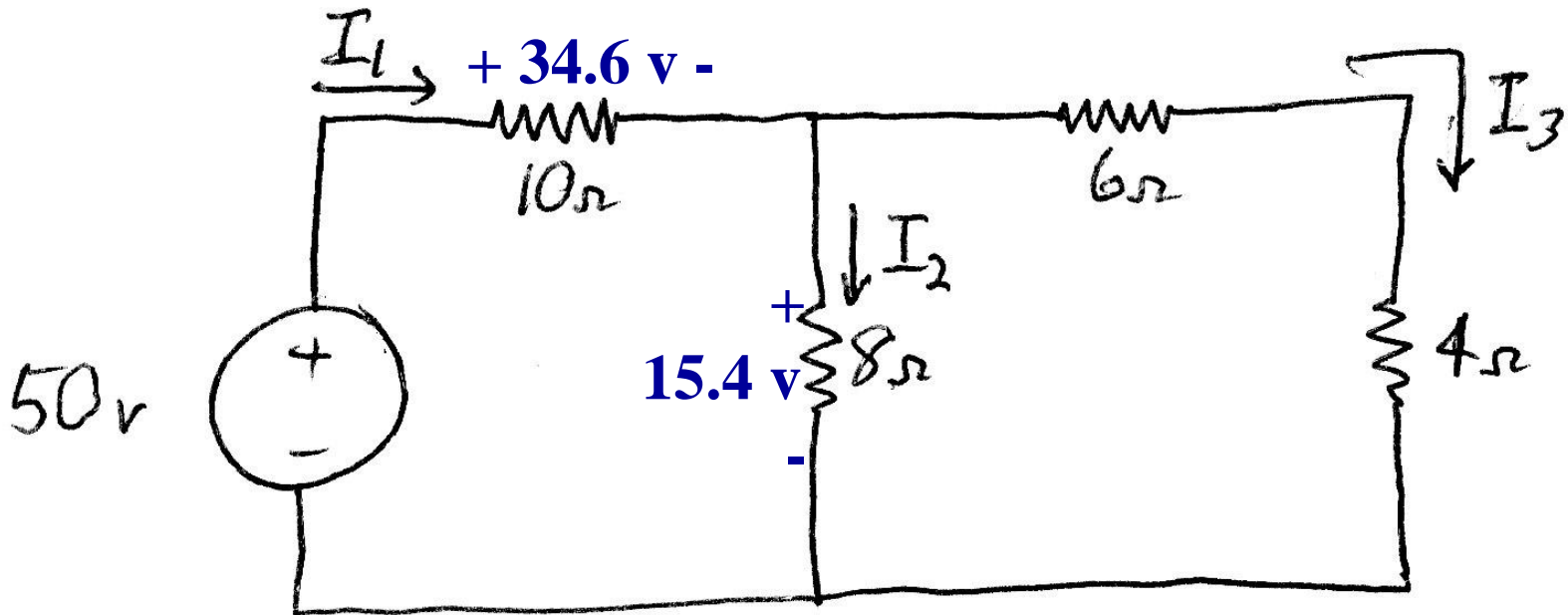

If $I_2 \cdot 8 \Omega = 15.4 \text{ v}$, then $I_2 = 15.4/8 = 1.93 \text{ A}$

By KCL, $I_1 - I_2 - I_3 = 0$, so $I_3 = I_1 - I_2 = 1.53 \text{ A}$