

OPERASIONAL AMPLIFIER (OP-AMP)

Komponen dasar sistem analog.

Penggunaan yang luas.


Fairchild Semiconductor 1965, μ A709.

Generasi kedua μ A709 atau 741.


MC1741, LM741, SN72741.

Standar industri dan komersil.

Simbol & Rangkaian internal

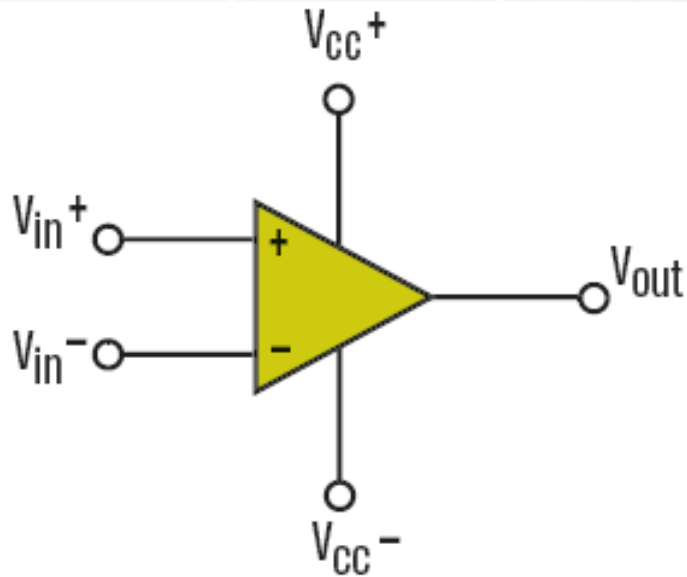



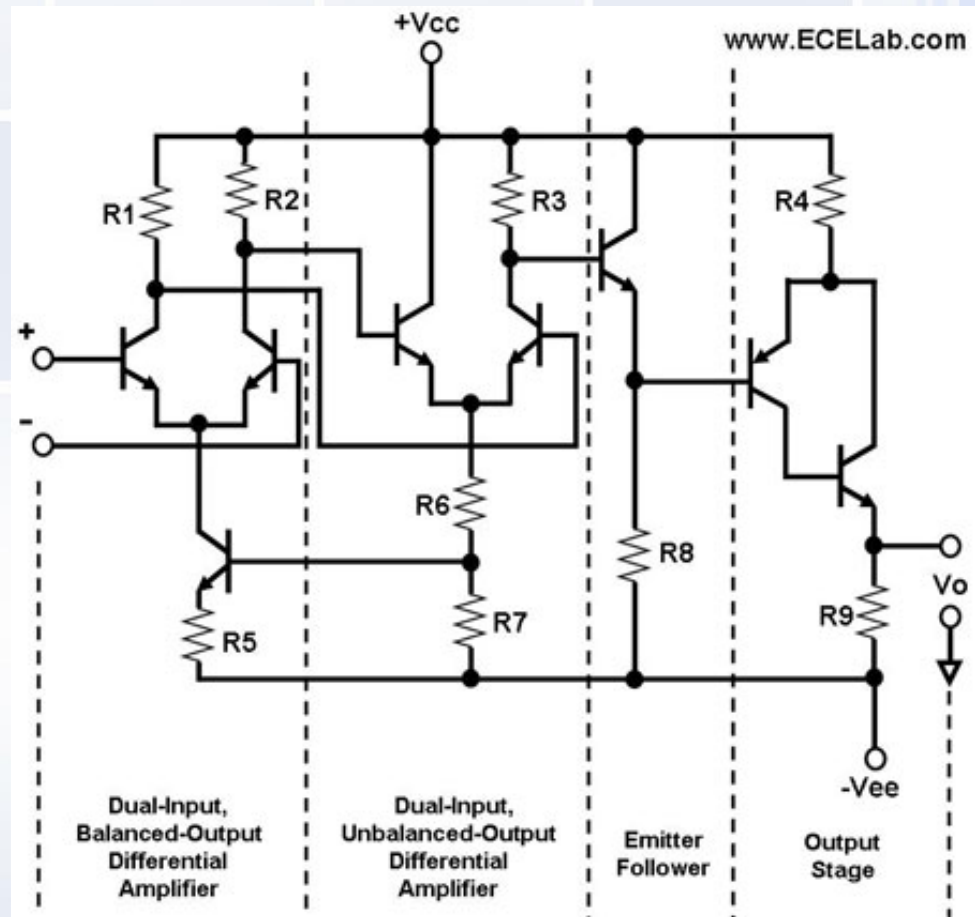
V_{in}^+ : non-inverting input
 V_{in}^- : inverting input
 V_{out} : output
 V_{CC}^+ : positive power supply
 V_{CC}^- : negative power supply




Karakteristik

Parameter	Ideal	LM741	LF347	LM318
Open-loop Gain (A_{OL})	∞	$2 \cdot 10^5$	10^5	$2 \cdot 10^5$
Input Resistance (R_{in})	$\infty \Omega$	2 M Ω	$10^{12} \Omega$	3 M Ω
Output Resistance (R_o)	0 Ω	75 Ω	75 Ω	75 Ω
Gain Bandwidth Product	∞ Hz	1 MHz	4 MHz	15 MHz
CMRR	∞	90 dB	100 dB	100 dB

Konstruksi

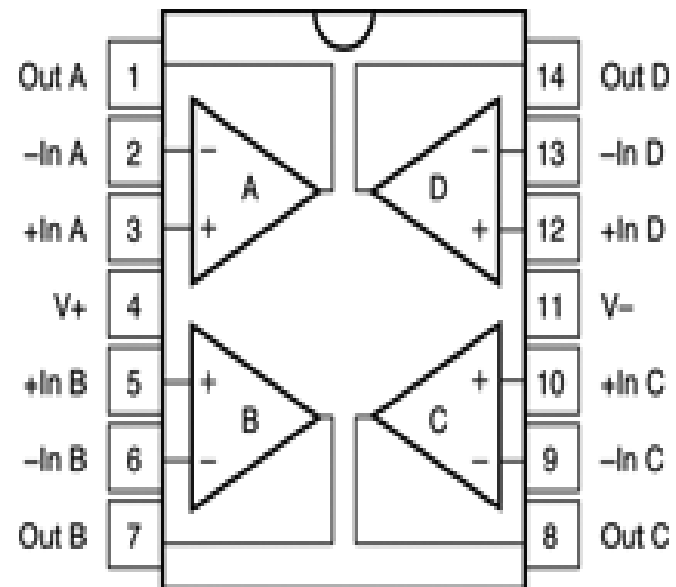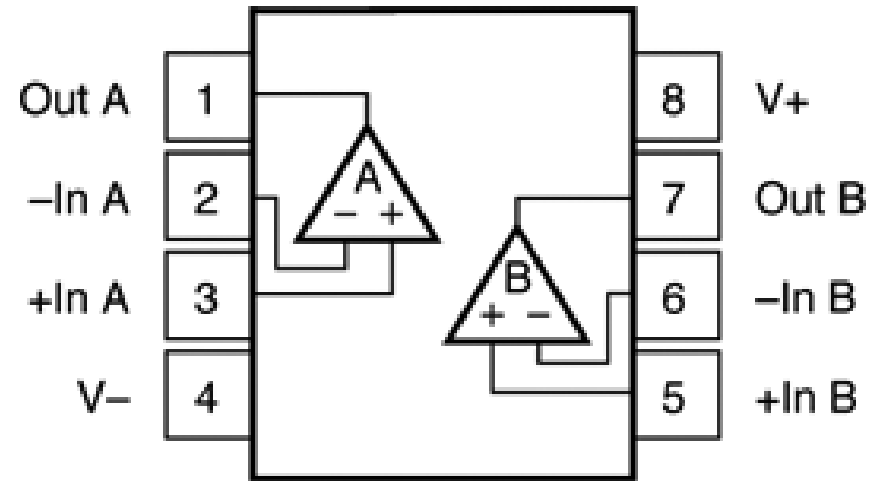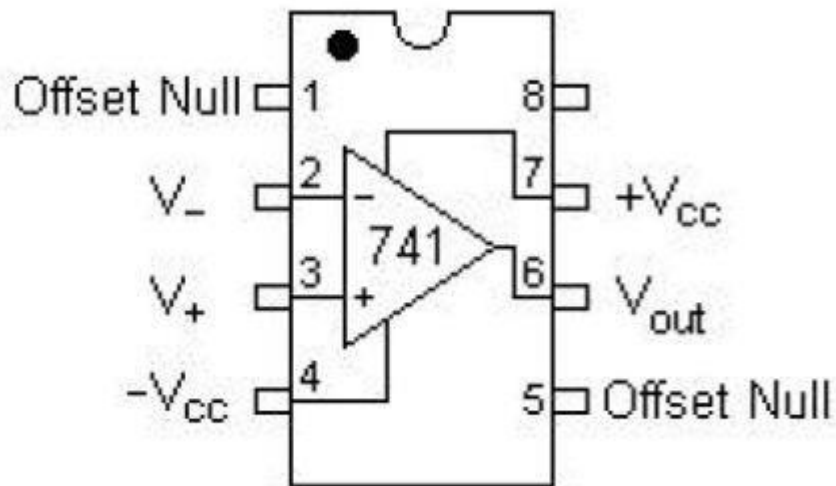


Inverting Amplifier

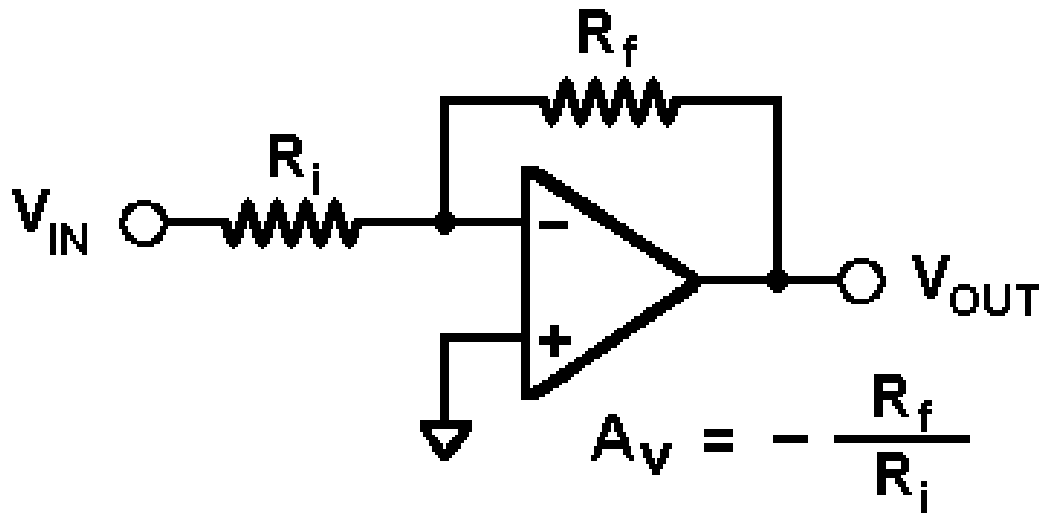

Resistansi input = R_s

Resistansi output ≈ 0


Non Inverting Amplifier

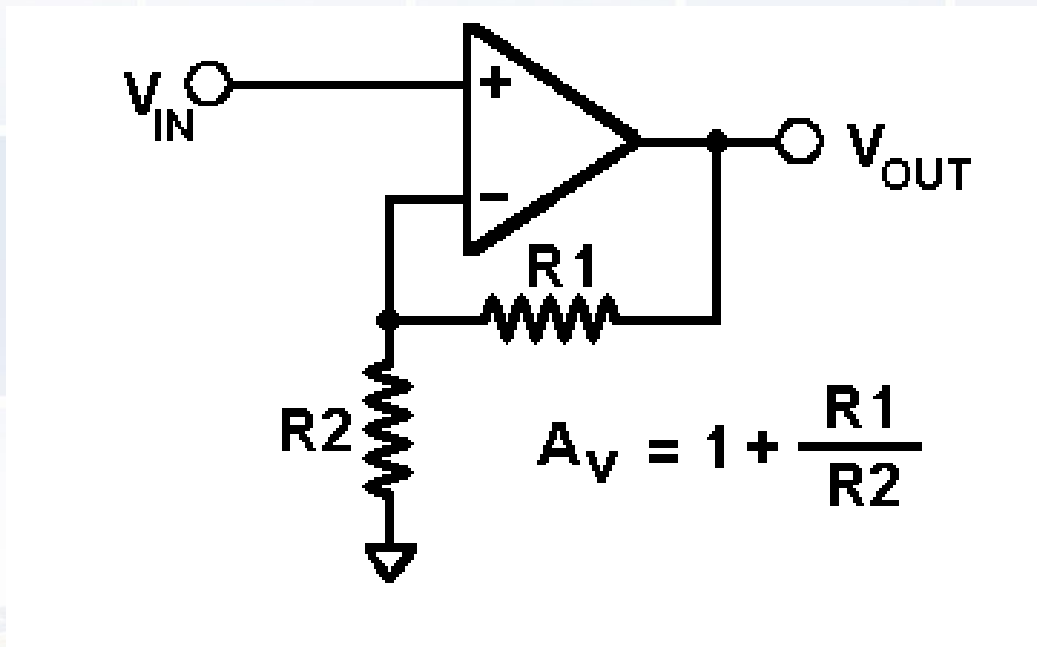

Resistansi input $\approx \infty$



Resistansi output ≈ 0

Penguatan = 1

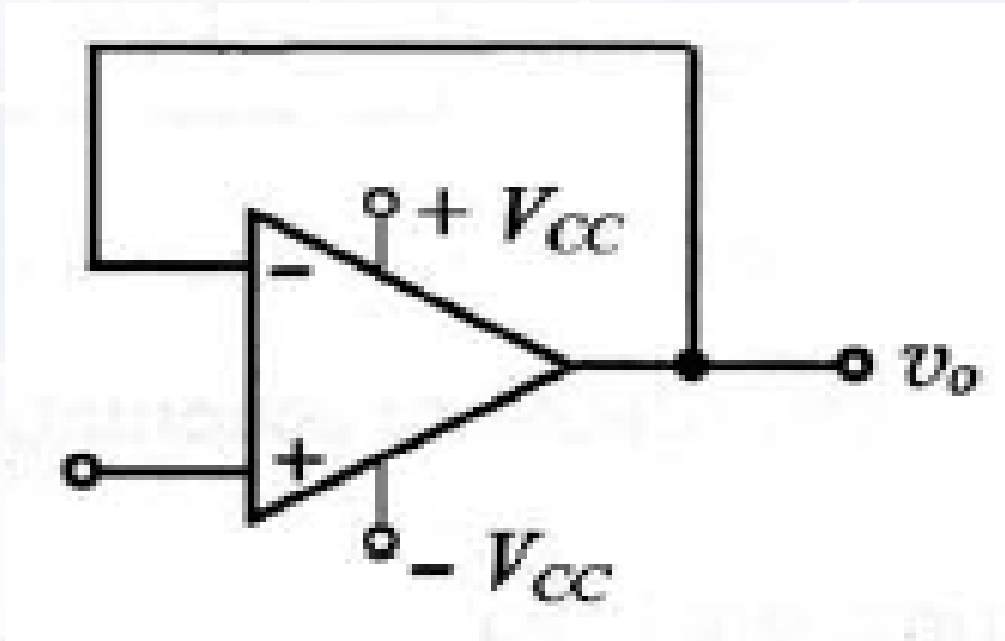

$$A_v = V_o/V_i = +1$$

Komparator

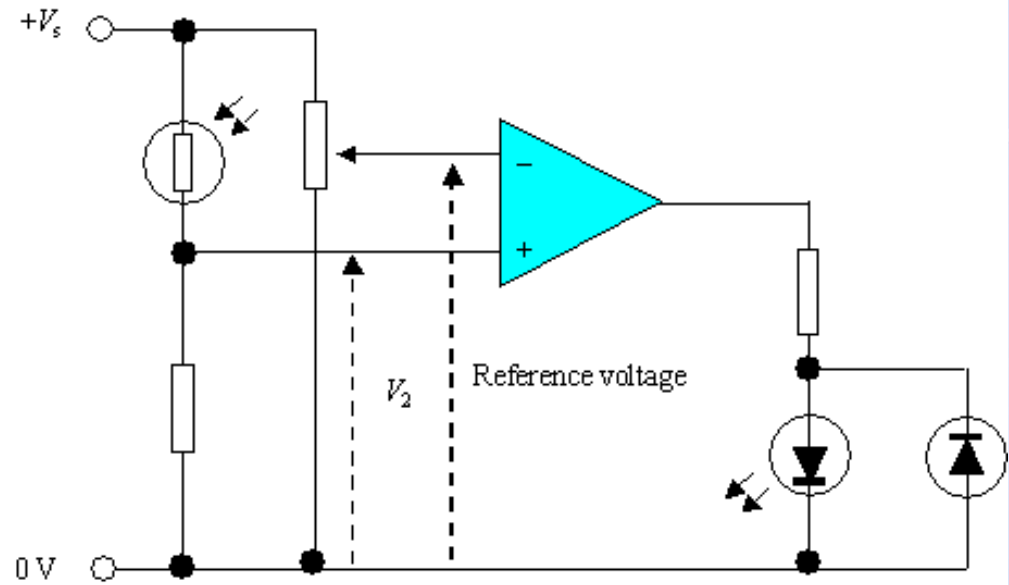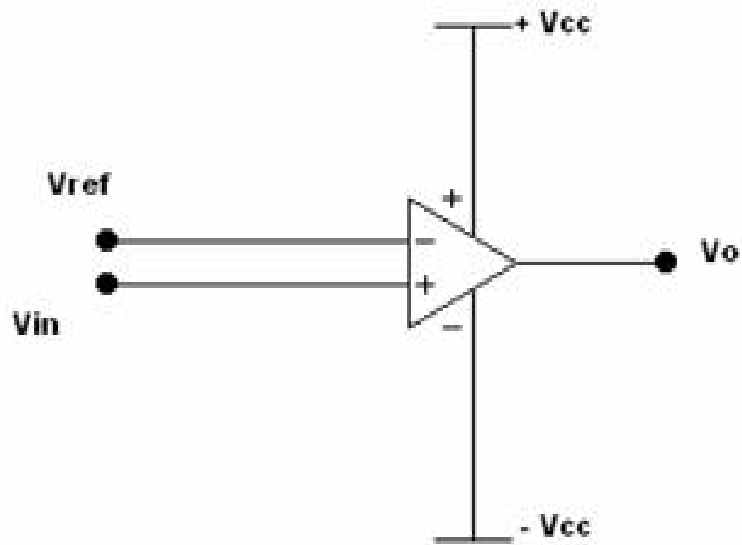

end

