

Bahan Ajar

Chapter 7



Materi Pembelajaran

Matakuliah :

DESAIN DAN SIMULASI RANGKAIAN ELEKTRONIKA

Kode Matakuliah : SKO 20425

Prodi : SISTEM KOMPUTER

Dosen Pengampu Matakuliah:

Bayu Nugroho, S.Kom., M.Eng

Tables of Content

Flip Flop

SR Flip Flop

Positive NAND Gate SR Flip-flop

The NOR Gate SR Flip-flop

Quad SR Bistable Latch 74LS279

Tugas Mandiri




Flip Flop (SR Flip Flop)

The SR flip-flop, also known as a SR Latch, can be considered as one of the most basic sequential logic circuit possible.


This simple flip-flop is basically a one-bit memory bistable device that has two inputs, one which will “SET” the device (meaning the output = “1”), and is labelled S and one which will “RESET” the device (meaning the output = “0”), labelled R.

Flip Flop (SR Flip Flop)

The Basic SR Flip-flop

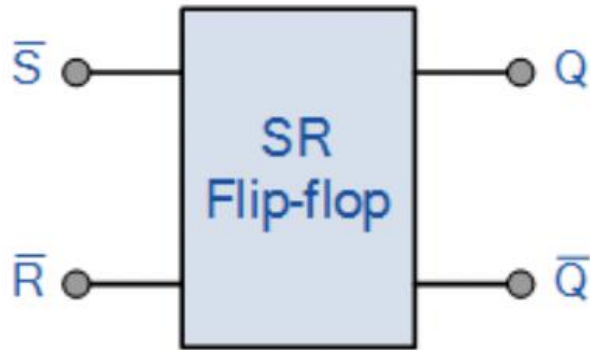

Symbol

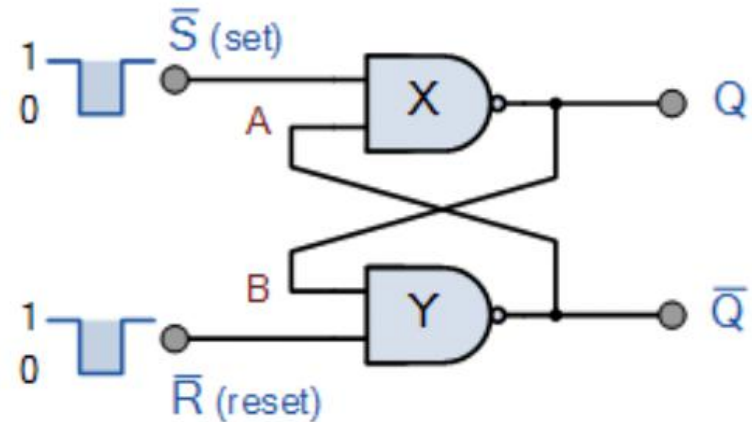

Circuit


Flip Flop (SR Flip Flop)

Truth Table for this Set-Reset Function

| State | S | R | Q | \bar{Q} | Description |
|---------|---|---|---|-----------|-----------------------|
| Set | 1 | 0 | 0 | 1 | Set $\bar{Q} \gg 1$ |
| | 1 | 1 | 0 | 1 | no change |
| Reset | 0 | 1 | 1 | 0 | Reset $\bar{Q} \gg 0$ |
| | 1 | 1 | 1 | 0 | no change |
| Invalid | 0 | 0 | 1 | 1 | Invalid Condition |


Flip Flop (SR Flip Flop)

S-R Flip-flop Switching Diagram

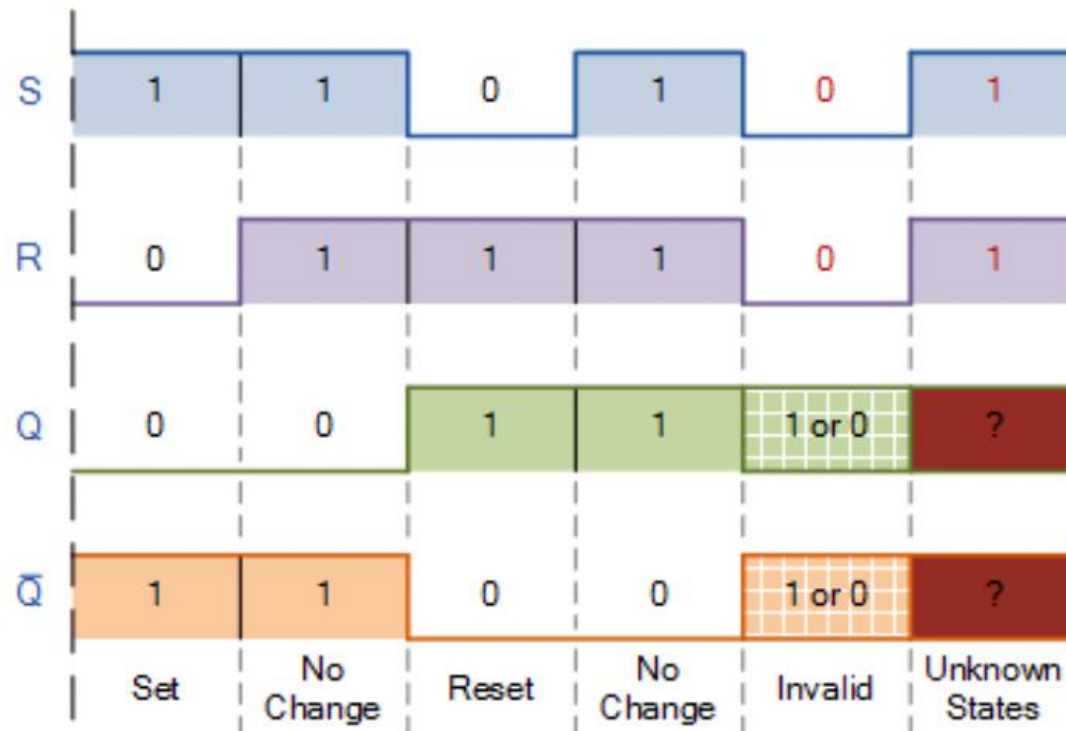

Positive NAND Gate SR Flip-flop

Positive NAND Gate SR Flip-flop

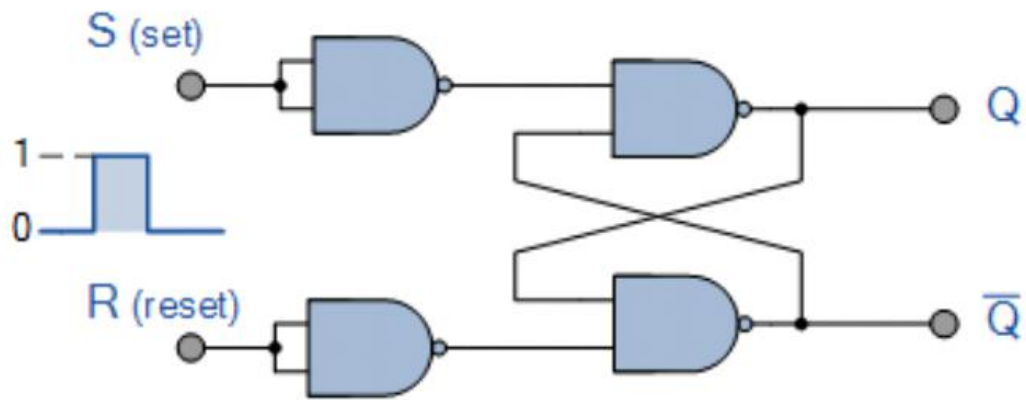


NAND Circuit

| S | R | Q | \bar{Q} |
|-----------|---|-----------|-----------|
| 0 | 0 | No change | |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | X | X |
| (Invalid) | | | |

Chapter 7

The NOR Gate SR Flip-flop

The NOR Gate SR Flip-flop

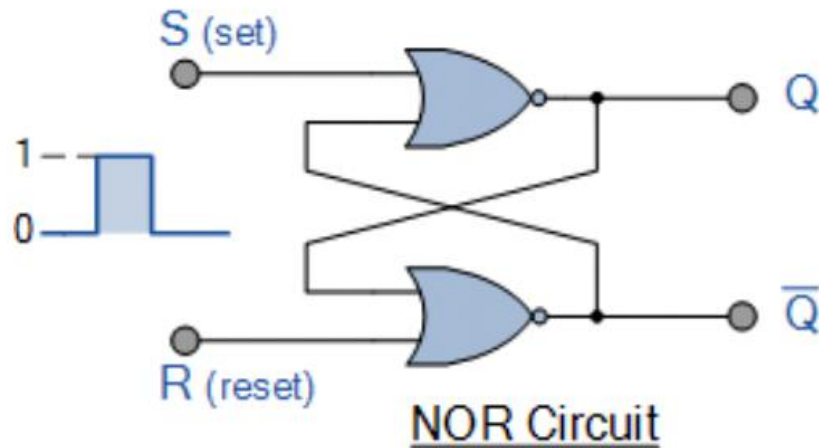


| S | R | Q | Q̄ |
|-----------|---|-----------|----|
| 0 | 0 | No change | |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | X | X |
| (Invalid) | | | |

Chapter 7

Quad SR Bistable Latch 74LS279

Quad SR Bistable Latch 74LS279

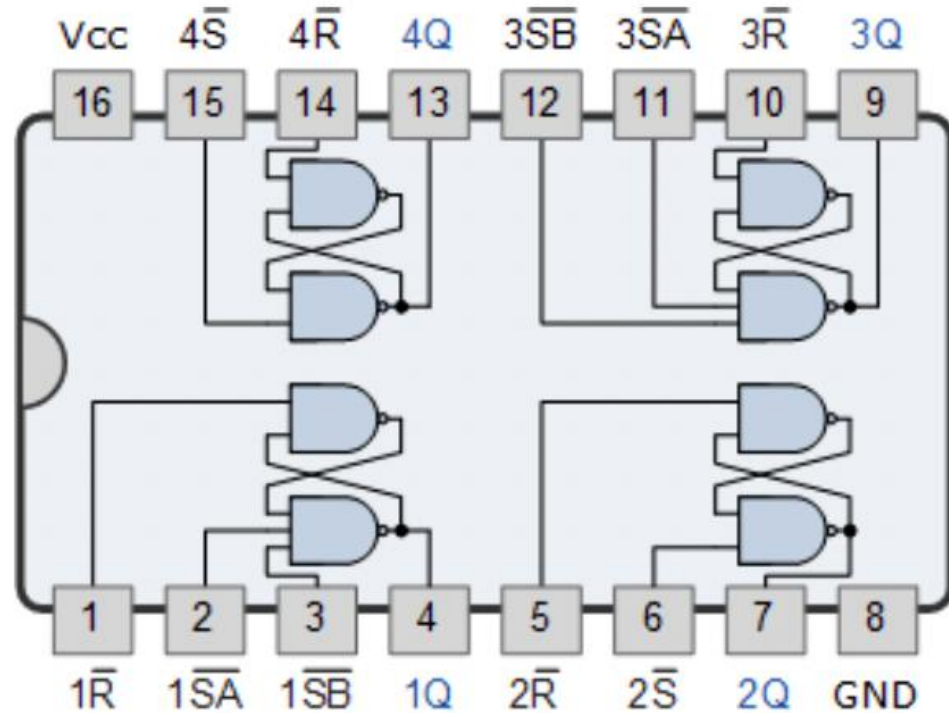

Chapter 7

Tugas Mandiri (teori):

Lakukan pembuatan skema rangkaian SR Flip Flop dengan LED menggunakan software simulator

Tugas Mandiri (prakt):

Lakukan Simulasi SR Flip Flop menggunakan software simulator dan jelaskan hasil simulasinya.

end

