

AC Circuit

- An AC circuit consists of a combination of circuit elements and an AC generator or source
- The output of an AC generator is sinusoidal and varies with time according to the following equation

$$- \Delta V = \Delta V_{\max} \sin 2\pi ft$$

- Δv is the instantaneous voltage
- ΔV_{\max} is the maximum voltage of the generator
- f is the frequency at which the voltage changes, in Hz

- Same thing about the current (if only a resistor)

$$- I = I_{\max} \sin 2\pi ft$$


Resistor in an AC Circuit

- Consider a circuit consisting of an AC source and a resistor
- The graph shows the current through and the voltage across the resistor
- The current and the voltage reach their maximum values at the same time
- The current and the voltage are said to be *in phase*
Voltage varies as

$$\Delta V = \Delta V_{\max} \sin 2\pi ft$$

Same thing about the current

$$I = I_{\max} \sin 2\pi ft$$

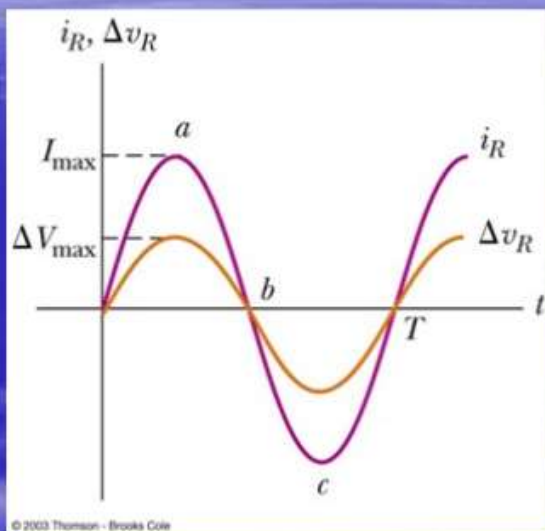

More About Resistors in an AC Circuit

- The direction of the current has no effect on the behavior of the resistor
- The rate at which electrical energy is dissipated in the circuit is given by

$$- P = i^2 R = (I_{\max} \sin 2\pi ft)^2 R$$

- where i is the *instantaneous current*
 - the heating effect produced by an AC current with a maximum value of I_{\max} is not the same as that of a DC current of the same value
 - The maximum current occurs for a small amount of time
- Averaging the above formula over one cycle we get

$$P = \frac{1}{2} I_{\max}^2 R$$

rms Current and Voltage

- The *rms current* is the direct current that would dissipate the same amount of energy in a resistor as is actually dissipated by the AC current

$$I_{\text{rms}} = \frac{I_{\max}}{\sqrt{2}} = 0.707 I_{\max}$$

- Alternating voltages can also be discussed in terms of rms values

$$\Delta V_{\text{rms}} = \frac{\Delta V_{\max}}{\sqrt{2}} = 0.707 \Delta V_{\max}$$

Ohm's Law in an AC Circuit


- rms values will be used when discussing AC currents and voltages
 - AC ammeters and voltmeters are designed to read rms values
 - Many of the equations will be in the same form as in DC circuits
- Ohm's Law for a resistor, R , in an AC circuit
 - $\Delta V_{\text{rms}} = I_{\text{rms}} R$
 - Also applies to the maximum values of v and i

Capacitors in an AC Circuit

- Consider a circuit containing a capacitor and an AC source
- The current starts out at a large value and charges the plates of the capacitor
 - There is initially no resistance to hinder the flow of the current while the plates are not charged
- As the charge on the plates increases, the voltage across the plates increases and the current flowing in the circuit decreases

More About Capacitors in an AC Circuit

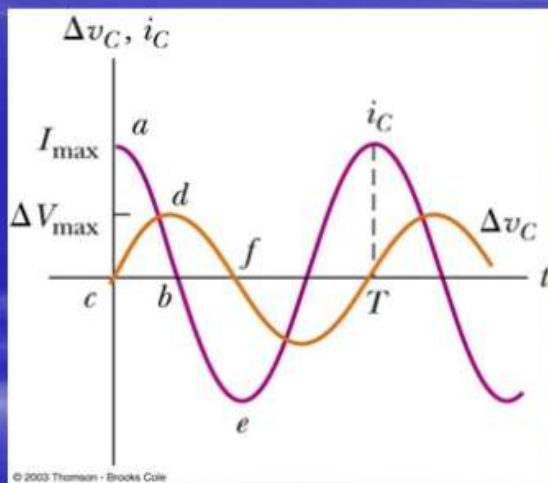- The current reverses direction
- The voltage across the plates decreases as the plates lose the charge they had accumulated
- The voltage across the capacitor lags behind the current by 90°



Capacitive Reactance and Ohm's Law


- The impeding effect of a capacitor on the current in an AC circuit is called the *capacitive reactance* and is given by

$$X_C = \frac{1}{2\pi fC}$$

- When f is in Hz and C is in F, X_C will be in ohms
- Ohm's Law for a capacitor in an AC circuit
 - $\Delta V_{\text{rms}} = I_{\text{rms}} X_C$

Inductors in an AC Circuit

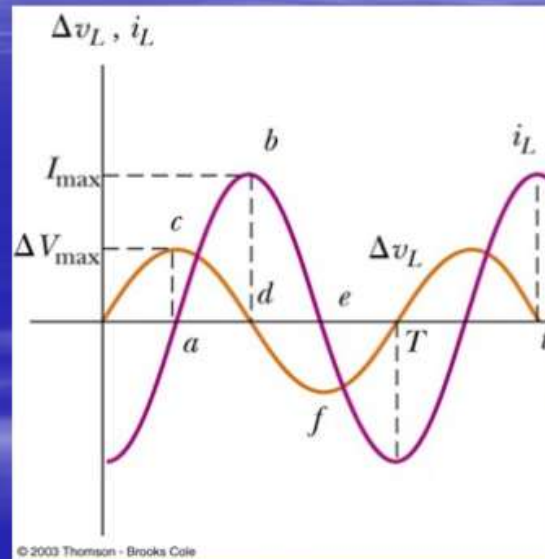- Consider an AC circuit with a source and an inductor
- The current in the circuit is impeded by the back emf of the inductor
- The voltage across the inductor always leads the current by 90°



Inductive Reactance and Ohm's Law

- The effective resistance of a coil in an AC circuit is called its *inductive reactance* and is given by
 - $X_L = 2\pi fL$
 - When f is in Hz and L is in H, X_L will be in ohms
- Ohm's Law for the inductor
 - $\Delta V_{\text{rms}} = I_{\text{rms}} X_L$