

### Example 33.1 **What Is the rms Current?**

The voltage output of an AC source is given by the expression  $\Delta v = (200 \text{ V}) \sin \omega t$ . Find the rms current in the circuit when this source is connected to a  $100\text{-}\Omega$  resistor.

$$\Delta V_{\text{rms}} = \frac{\Delta V_{\text{max}}}{\sqrt{2}} = \frac{200 \text{ V}}{\sqrt{2}} = 141 \text{ V}$$

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{R} = \frac{141 \text{ V}}{100 \text{ }\Omega} = 1.41 \text{ A}$$

### Example 33.2 A Purely Inductive AC Circuit

In a purely inductive AC circuit,  $L = 25.0 \text{ mH}$  and the rms voltage is 150 V. Calculate the inductive reactance and rms current in the circuit if the frequency is 60.0 Hz.

$$\begin{aligned} X_L &= \omega L = 2\pi fL = 2\pi(60.0 \text{ Hz})(25.0 \times 10^{-3} \text{ H}) \\ &= 9.42 \Omega \end{aligned}$$

$$I_{\text{rms}} = \frac{\Delta V_{L,\text{rms}}}{X_L} = \frac{150 \text{ V}}{9.42 \Omega} = 15.9 \text{ A}$$

### Example 33.3 A Purely Capacitive AC Circuit

An  $8.00\text{-}\mu\text{F}$  capacitor is connected to the terminals of a  $60.0\text{-Hz}$  AC source whose rms voltage is  $150\text{ V}$ . Find the capacitive reactance and the rms current in the circuit.

$$\omega = 2\pi f = 377\text{ s}^{-1}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(377\text{ s}^{-1})(8.00 \times 10^{-6}\text{ F})} = 332\ \Omega$$

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{X_C} = \frac{150\text{ V}}{332\ \Omega} = 0.452\text{ A}$$