
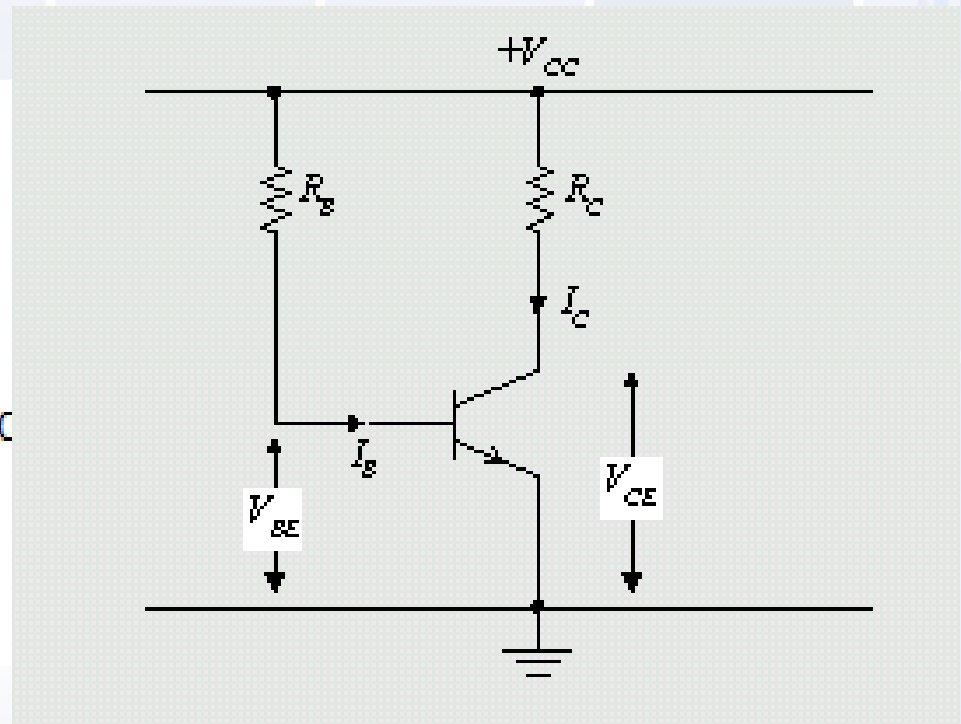


Bias Transistor

Bias Basis

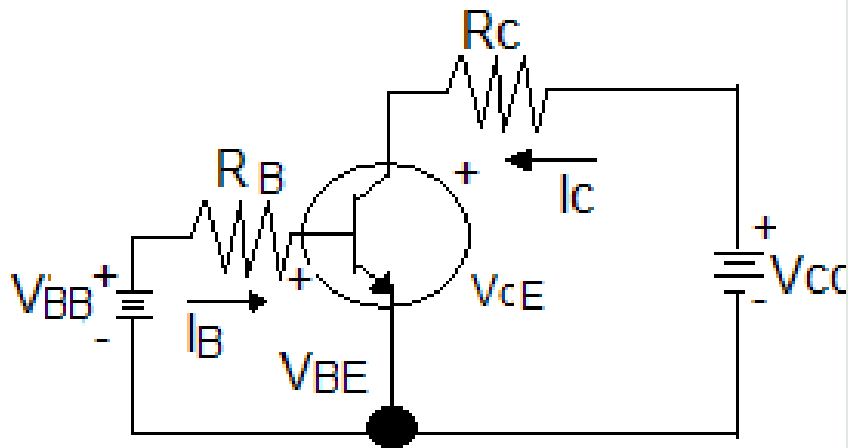

Tegangan kolektor-emitor cutoff : $V_{CE} = V_{CC}$

Arus kolektor saturasi : $I_C = \frac{V_{CC}}{R_C}$

Arus Basis : $I_B = \frac{V_{BB} - V_{BE}}{R_B}$

Arus Kolektor aktif : $I_C = I_B \beta_{dc}$

Tegangan kolektor-emitor aktif : $V_{CE} = V_{CC} - I_C R_C$

Contoh 1.

**Sebuah rangkaian transistor bias basis,
 $V_{CC} = 10 \text{ V}$, $R_B = 330 \text{ k}\Omega$, $R_C = 470 \text{ }\Omega$,
transistor dengan $\beta_{dc} = 200$.**

Tentukanlah Q point



Jawab

Diketahui :

$$V_{CC} = 10 \text{ V}, R_B = 330 \text{ k}\Omega, R_C = 470 \Omega, \beta_{dc} = 200.$$

Di tanya : Q point


$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{10 - 0,7}{330\text{k}} = 28,2 \mu\text{A}.$$

$$I_C = I_b \beta_{dc} = 28,2 \mu\text{A} \cdot 200 = 5,64 \text{ mA}.$$

$$V_{CE} = V_{CC} - I_C R_C = 10 - 5,64\text{mA} \cdot 470 = 7,35 \text{ V}.$$

V_{CE} cut of = $V_{CC} = 10$ V.

I_C saturasi = $V_{CC}/R_C = 10/470 = 21,27$ mA

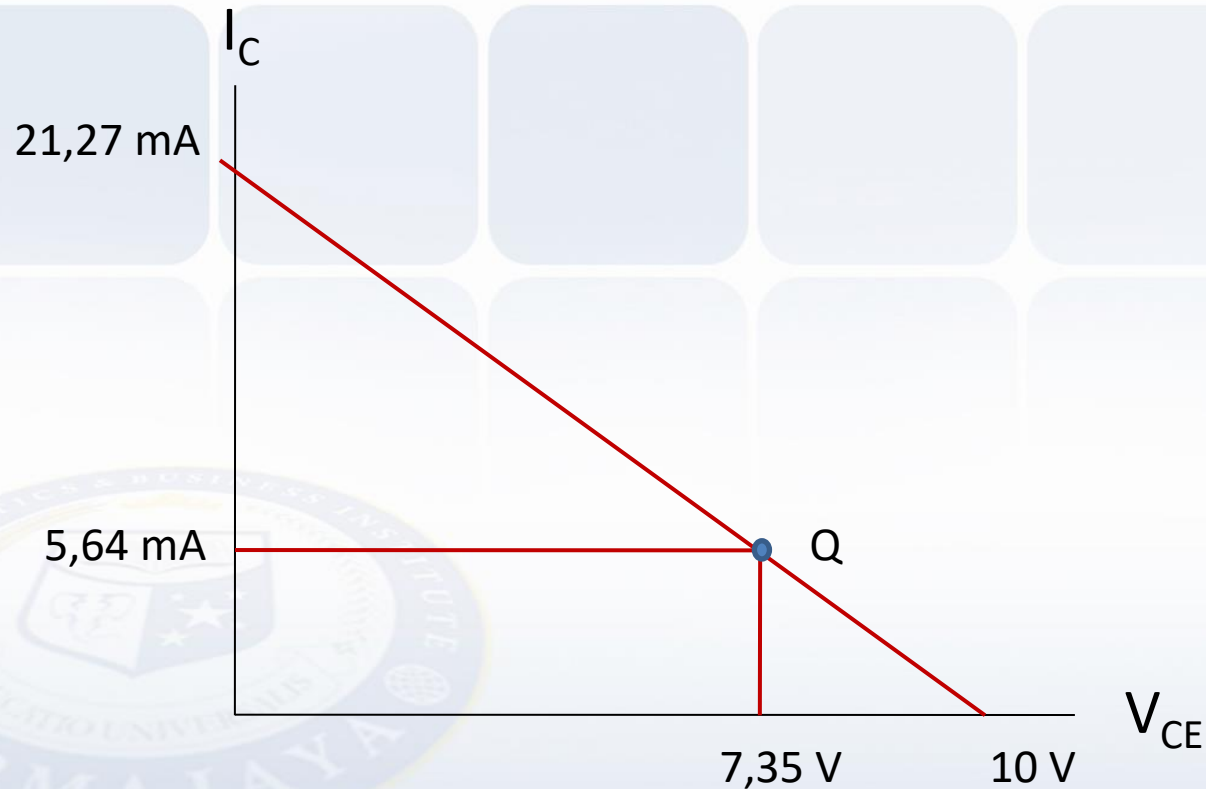

Contoh 2.

**Sebuah rangkaian transistor bias basis,
 $V_{CC} = 15 \text{ V}$, $R_B = 500 \text{ k}\Omega$, $R_C = 3 \text{ k}\Omega$,
transistor dengan $\beta_{dc} = 100$.**

Tentukanlah Q point



Jawab

Diketahui :

$$V_{CC} = 15, R_B = 500 \text{ k}\Omega, R_C = 3 \text{ k}\Omega, \beta_{dc} = 100.$$

Di tanya : Q point


$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{15 - 0,7}{500 \text{ k}} = 28,6 \text{ }\mu\text{A}.$$

$$I_C = I_B \beta_{dc} = 28,6 \text{ }\mu\text{A} \cdot 100 = 2,86 \text{ mA}.$$

$$V_{CE(\text{aktif})} = V_{CC} - I_C R_C = 15 - 2,86 \text{ mA} \cdot 3 \text{ k}\Omega = 6,5 \text{ V}.$$

V_{CE} cut of = $V_{CC} = 15$ V.

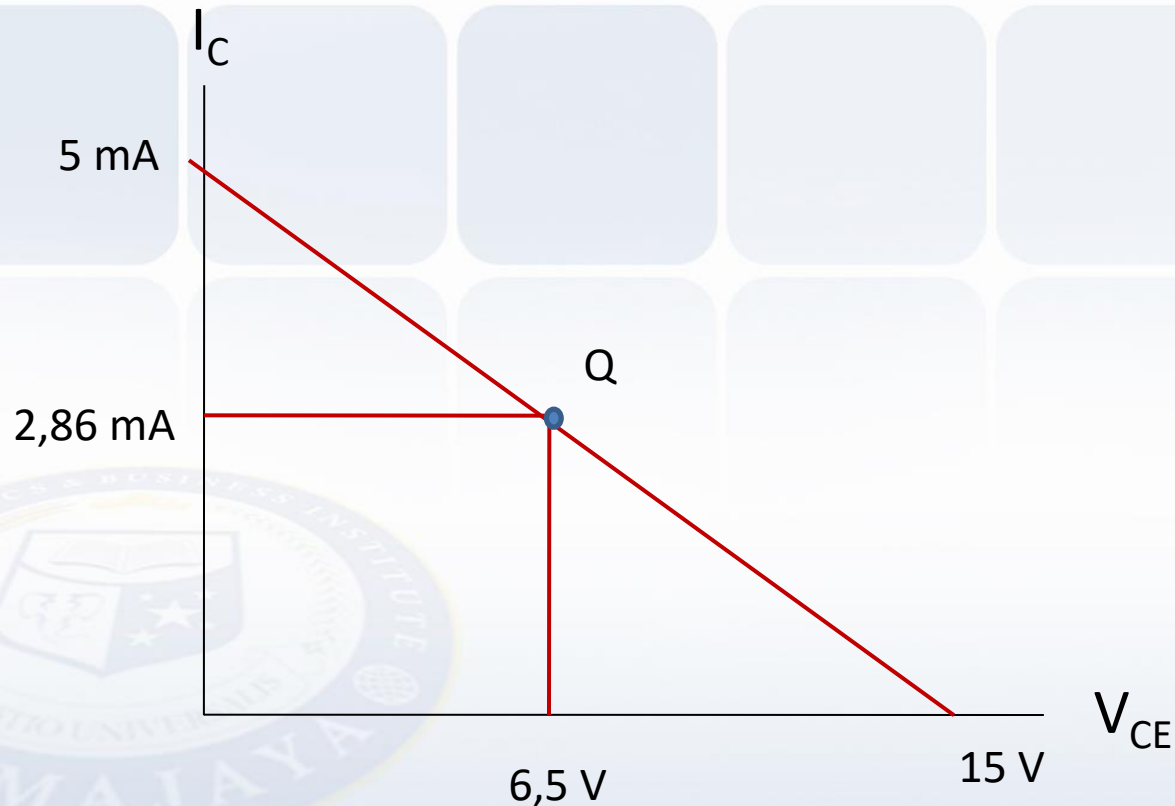I_C saturasi = $V_{CC}/R_C = 15/3$ k Ω = 5 mA



end

